


ECE 6130 LECTURE 5

Text Section: 2.5,6


Portfolio: For a terminated lossless transmission line:

- 1) Describe how to find the voltage at any point on the line as a function of time
- 2) Describe how to find the voltage along the line at any point in time.

TRANSIENTS ON TRANSMISSION LINES

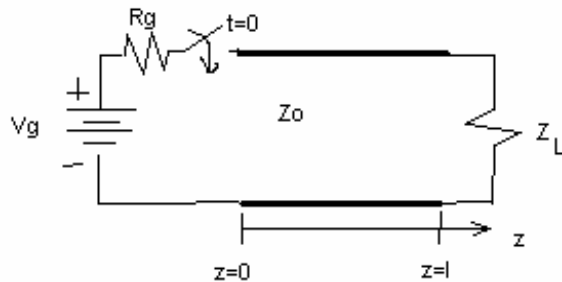

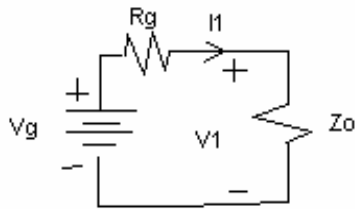
Note definition of z axis is different from previous work.



Equivalent circuit at initial time ($t=0$)

The switch is closed, no voltage has moved down the transmission line.
All the generator “sees” is Z_0 ... Z_L is too far away.

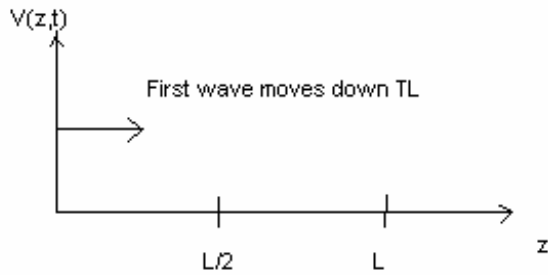
$$I_1^+ = V_g / (R_g + Z_0) \leftarrow + \text{ means positive-traveling wave, “1” means first wave}$$
$$V_1^+ = I_1^+ Z_0 = V_g Z_0 / (R_g + Z_0)$$



Velocity of wave $v_p = 1 / \sqrt{\epsilon\mu}$

Wave moves down TL with no reflections until it reaches the load ...

Time to reach load: $T = L / v_p$

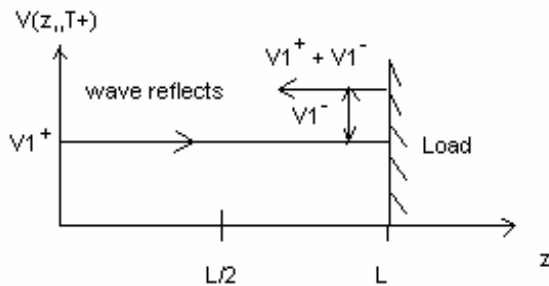


Wave reflects off load and starts back.

$$V_1^- = \Gamma_L V_1^+$$

$$\Gamma_L = (Z_L - Z_0) / (Z_L + Z_0)$$

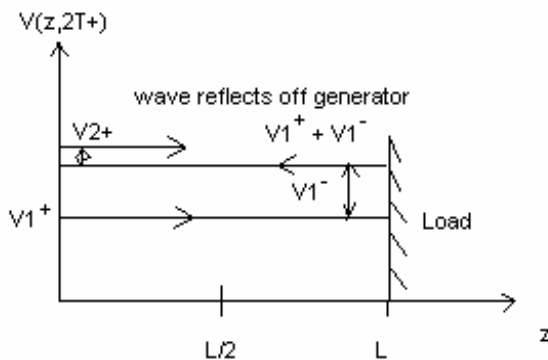(For $Z_L = 2 Z_0$, $\Gamma_L = 1/3 \leftarrow$ This is real ... what happens if it is complex? Get phase change as well as reflection.)



Wave V_1^- now reflects off generator.

New +-traveling wave is produced:

$$V_2^+ = \Gamma_g V_1^-$$

$$\Gamma_g = (Z_g - Z_0) / (Z_g + Z_0)$$

Notice that reflections are getting progressively smaller.

Waves keep reflecting until STEADY STATE is reached:


(additional reflections are negligibly small)

$V_{\infty} = V_g Z_L / (R_g + Z_L)$ ← Voltage on line at steady state.


This is the SAME as we would have observed in the DC case!

$I_{\infty} = V_{\infty} / Z_L = V_g / (R_g + Z_L)$

BOUNCE DIAGRAMS

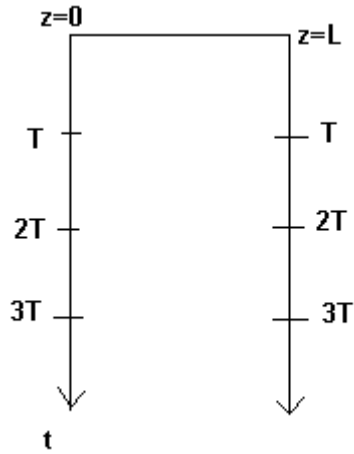

Axes: Time and distance

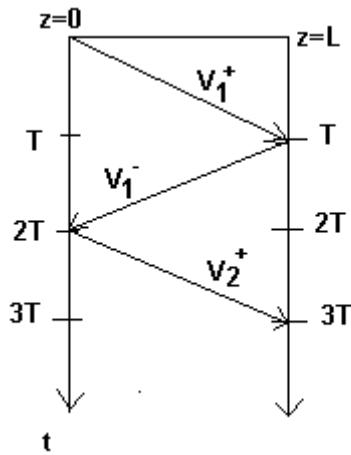

$$V_1^- = \Gamma_L V_1^+$$



$$V_2^+ = \Gamma_g V_1^- = \Gamma_g \Gamma_L V_1^+$$

$$V_2^- = \Gamma_L V_2^+ = \Gamma_g \Gamma_L^2 V_1^+$$

How to find $V(z,t)$ for any z and t :

1. Find the point (z,t) on the bounce diagram (eg. $Z = L/2, t = 3T$)
2. Draw a line back to $T=0$

3. Add up all of the V traces you cross

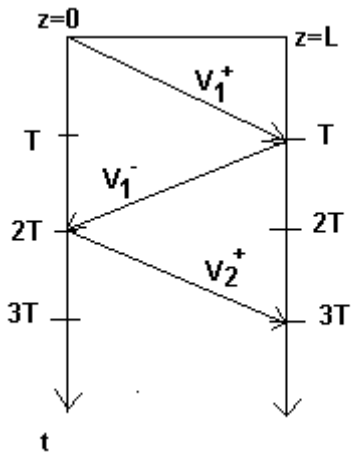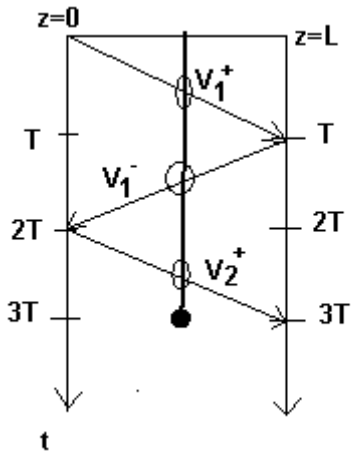

$$V(L/2, 3T) = V_1^+ + V_1^- + V_2^+$$

Example : Handout