 


## The Spartan 3e FPGA

## The Spartan 3e FPGA

- ◆ What's inside the chip?
  - How does it implement random logic?
  - What other features can you use?
- ◆ What do all these things mean?
  - LUT, Slice, BRAM, DCM, IOB, CLB...
- ◆ Two important documents  
(linked to the class web site)
  - Spartan3e Family Complete Data Sheet
  - Spartan3e User Guide


# What's on the chip?



CS/EE 3710

00312-1\_01\_032606

# What's on the chip?

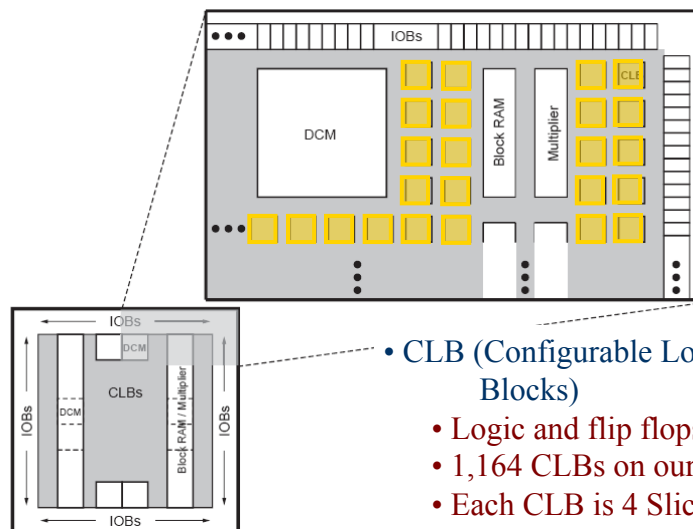


• CLB (Configurable Logic Blocks)

- Logic and flip flops
- 1,164 CLBs on our chip
- Each CLB is 4 Slices
- 500k total “system gates”

CS/EE 3710


## What's on the chip?

 

- IOB (Input Output Blocks)
  - Communicate off chip
  - Our chip has 232 total pins in a 320 BGA package

CS/EE 3710

## What's on the chip?

 


- BRAM (Block RAM)
  - On-chip SRAM
  - 18k bits per block
  - 20 blocks on our chip

CS/EE 3710

DS312-1\_01\_032605

## What's on the chip?

 


- Multiplier
  - Custom 18x18 multiplier
  - One per RAM block...

CS/EE 3710

DS312-1\_01\_032606

## What's on the chip?

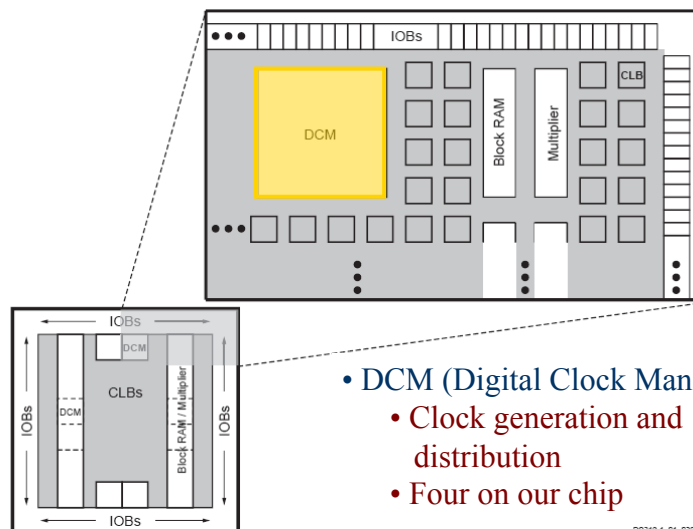


- DCM (Digital Clock Manager)
  - Clock generation and distribution
  - Four on our chip

CS/EE 3710

DS312-1\_01\_032606

# What's on the chip?

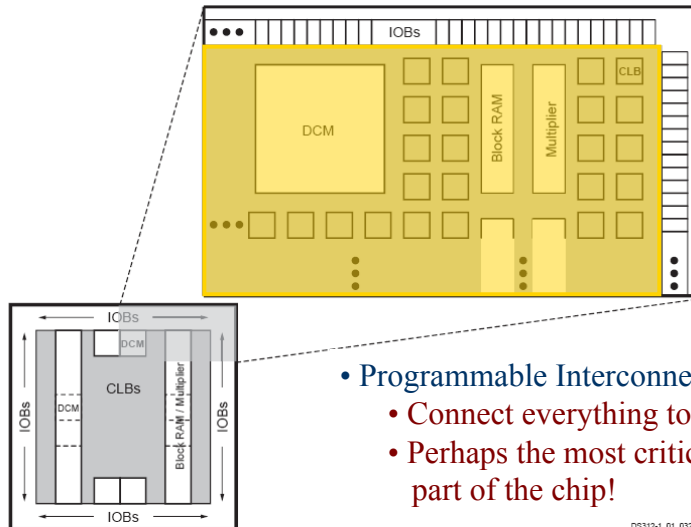


- Programmable Interconnect
  - Connect everything together
  - Perhaps the most critical part of the chip!

CS/EE 3710

DS312-1\_01\_032606
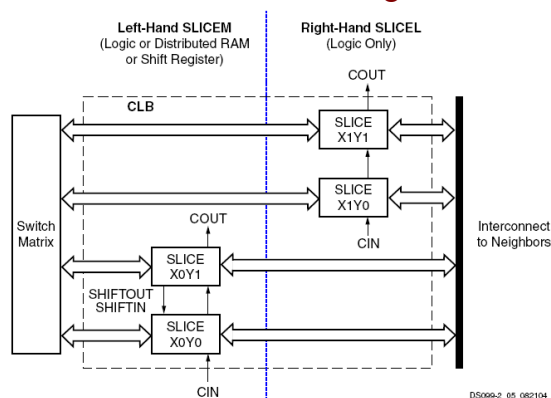
# CLB: Configurable Logic Block

- ◆ 4 “Slices” per CLB
  - The slices work together to make logic, flip flops, distributed RAM, or shift registers
  - Connected to other CLBs through Switch Matrix





CS/EE 3710

DS099-2\_05\_082104

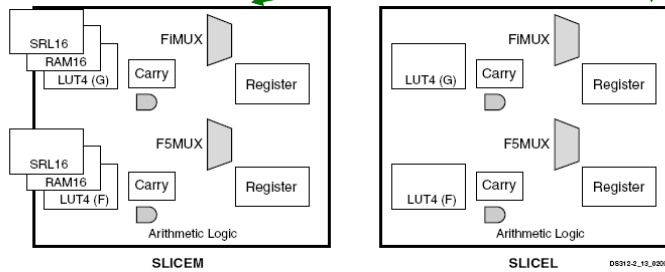 
# Left and Right Slices

- ◆ SRL16 = 16-bit shift register
- ◆ RAM16 = 16-bit RAM (16x1 bit memory)
- ◆ LUT4 = four-bit lookup table (16x1 bit memor)
- ◆ SLICEM = slice that can be memory or logic
- ◆ SLICEL = slice that can only be logic



CS/EE 3710


## What's Really in a Slice?

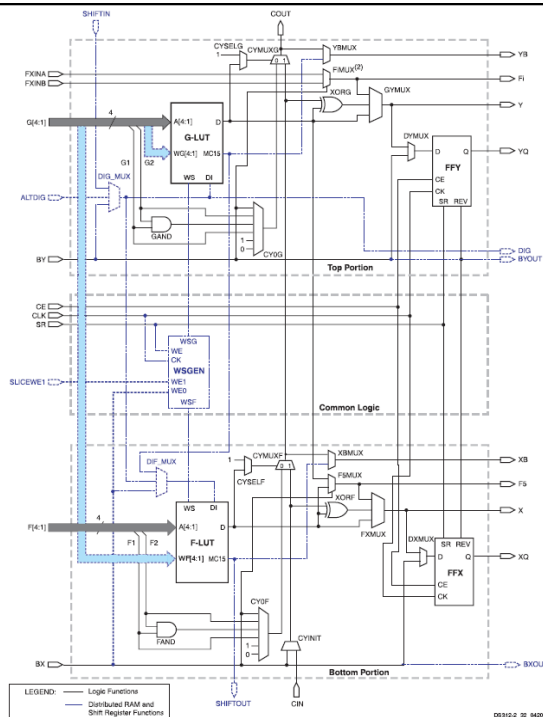

CS/EE 3710
 
## LUT 4 – Basic Building Block


- RAM memory 4-bit input, 1-bit output
- Can implement any logic function of up to 4 inputs




Patrick Schaumont  
Spring 2008

## LUT 4 – Basic Building Block

 - Example: Implement 3-input AND
- Assume A0 - A2 are used





A0	A1	A2	A3	Q
0	0	0	x	0
0	0	1	x	0
0	1	0	x	0
0	1	1	x	0
1	0	0	x	0
1	0	1	x	0
1	1	0	x	0
1	1	1	x	1

 



Patrick Schaumont  
Spring 2008

# Slice Muxes extend LUT4

  

Patrick Schaumont  
Spring 2008


# Once CLB – up to LUT7

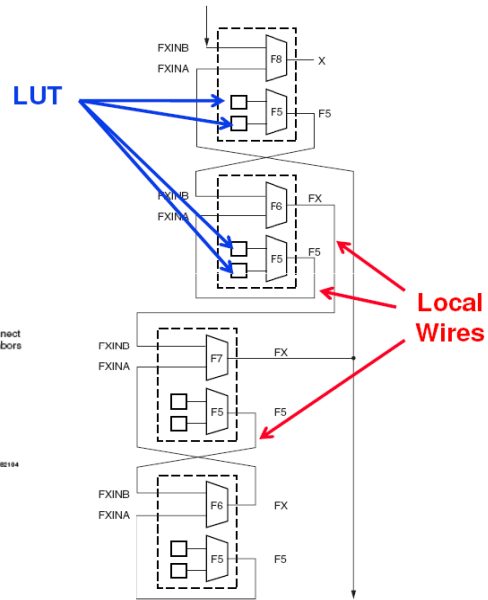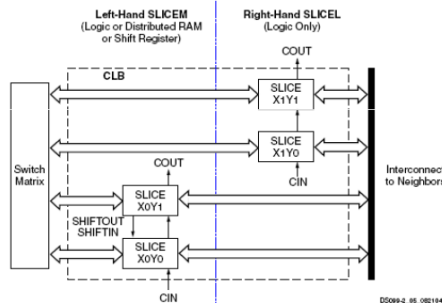


Patrick Schaumont  
Spring 2008




# Top Half of a SliceM (left)

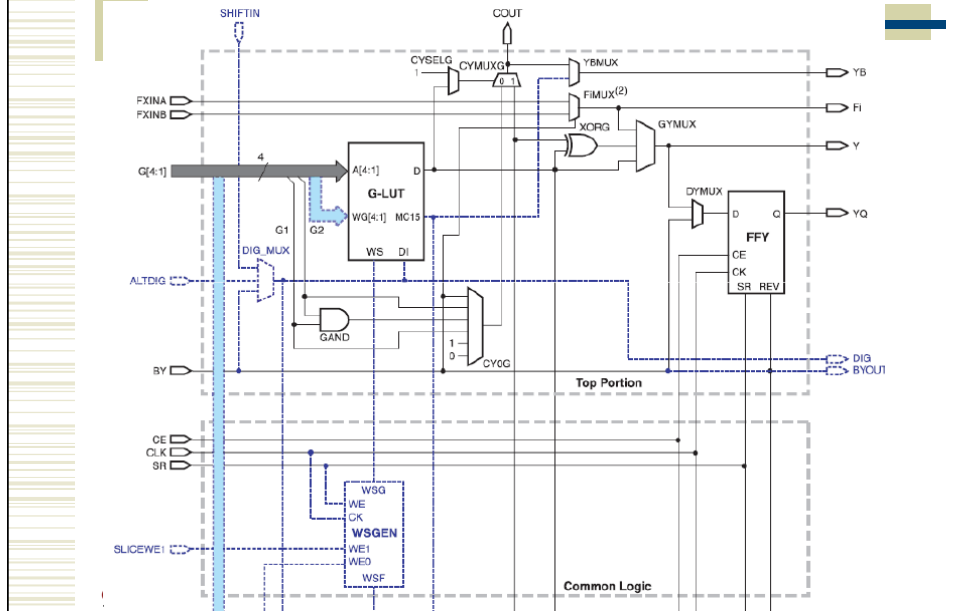


# Top Half of a SliceM (left)

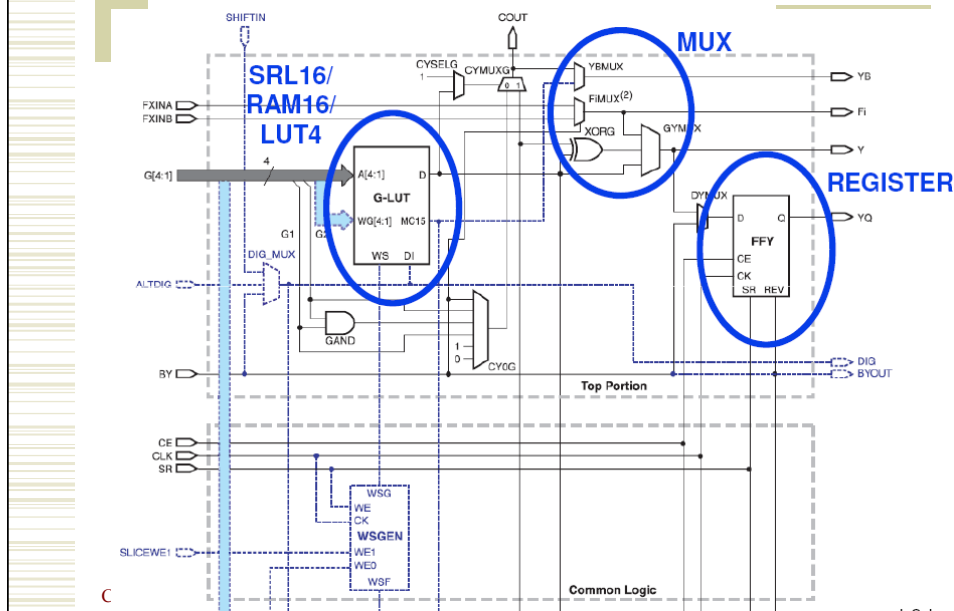


# Logic-only (combinational)

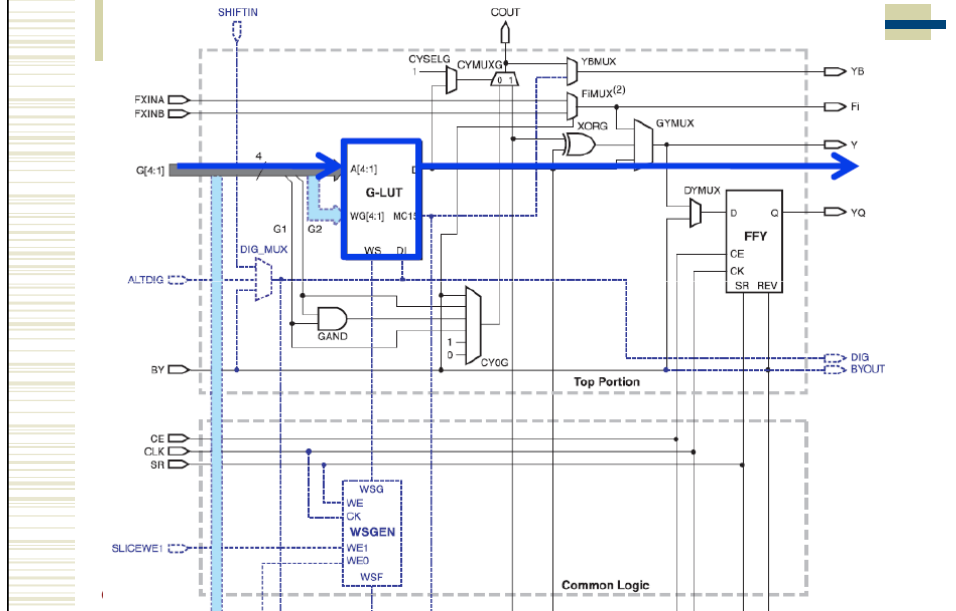


# Logic + register (sequential)

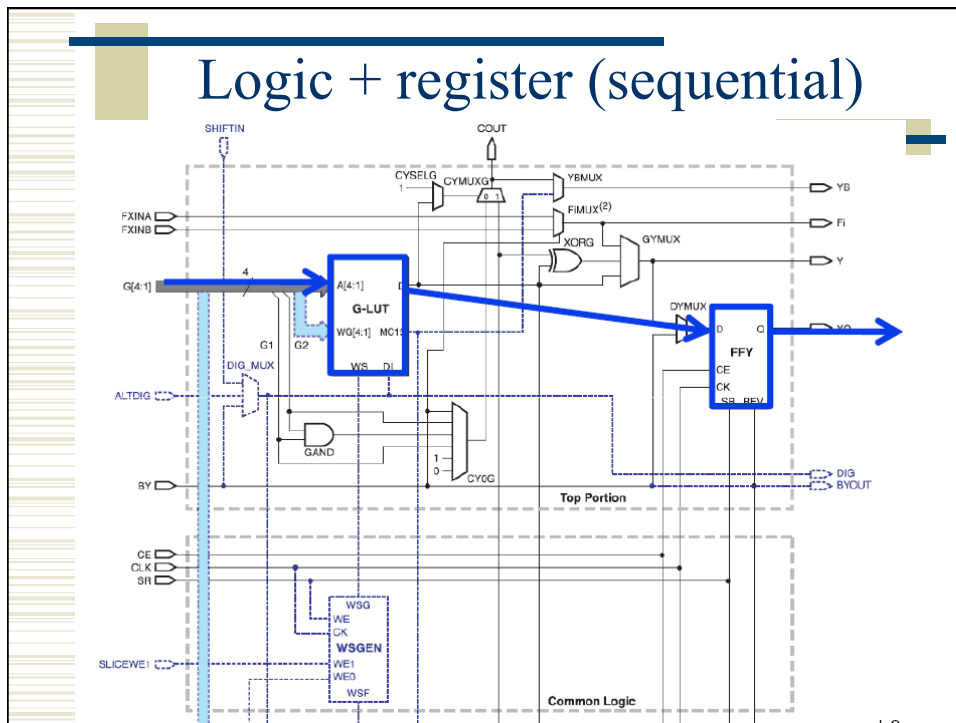


# Just register

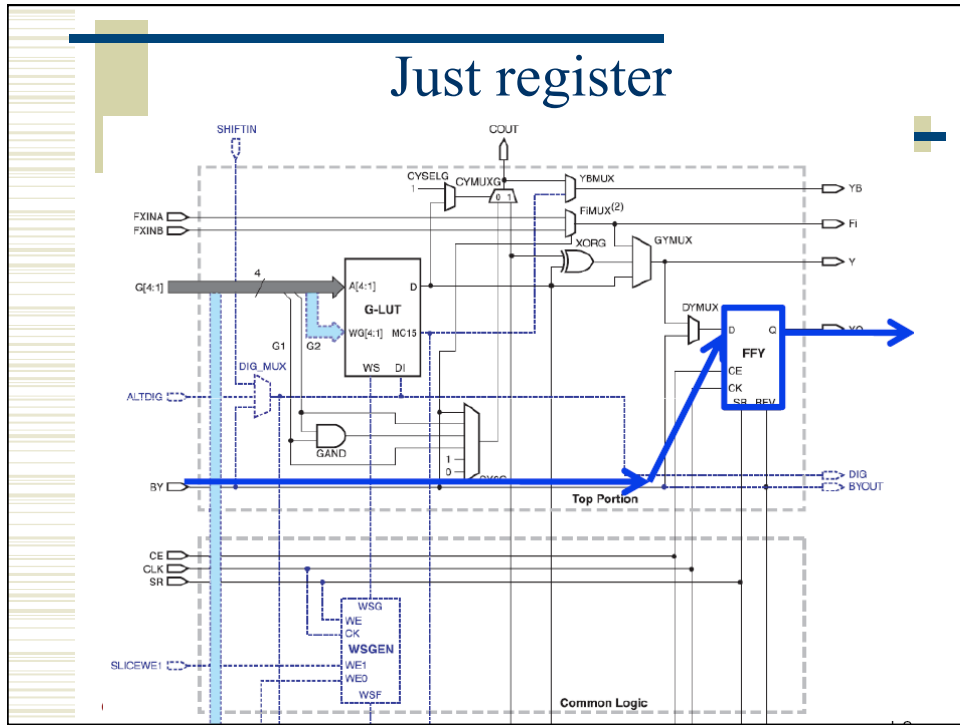

# Fast Carry Path (arithmetic)

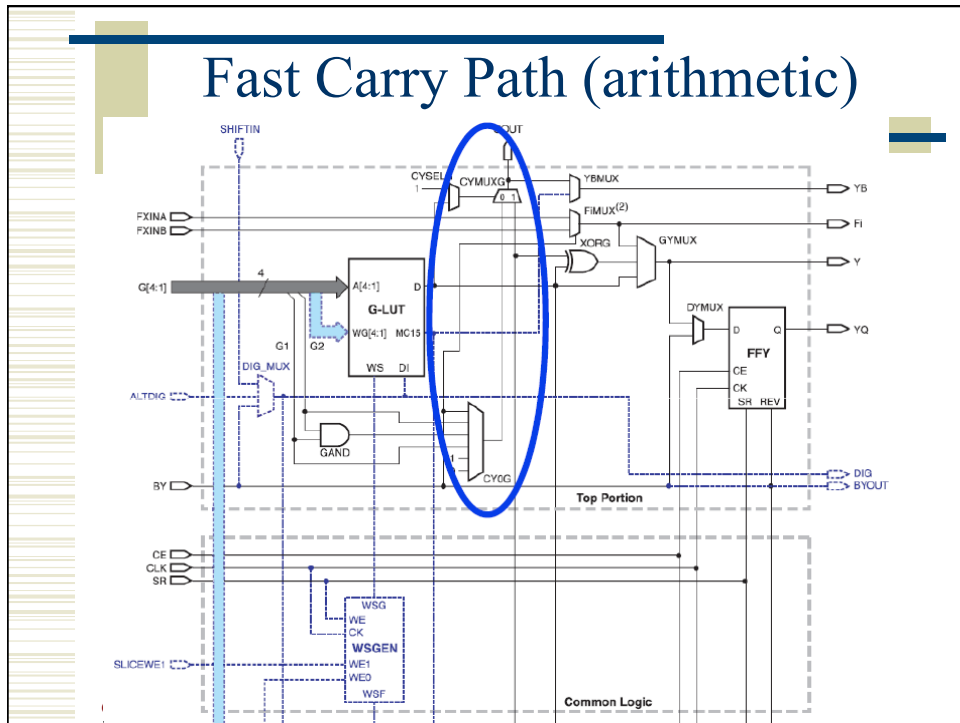


# Fast Carry Path (arithmetic)

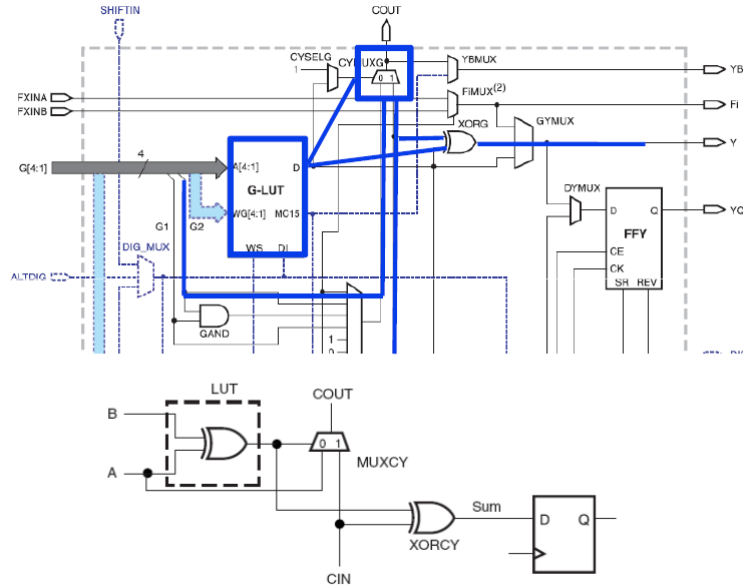

DS312-2\_37\_021305


# Fast Carry Path (arithmetic)

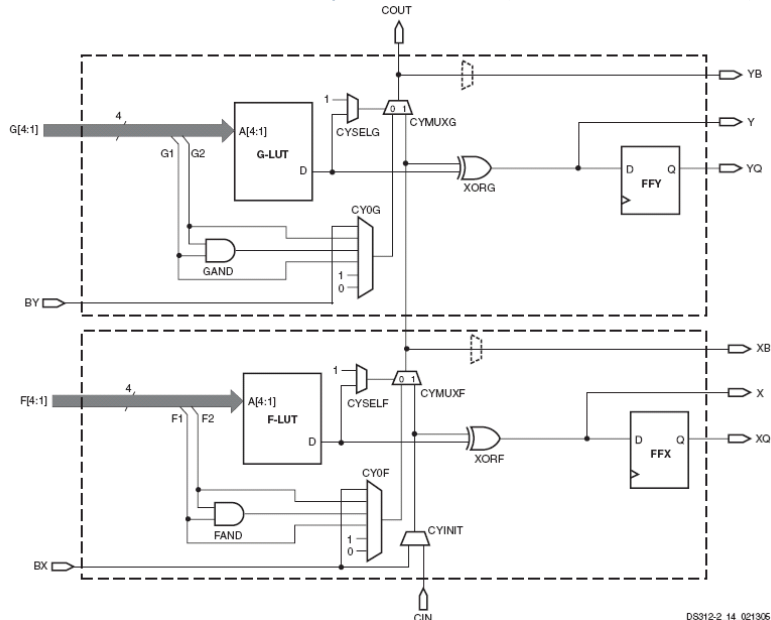

DS312-2\_14\_021306
 
## Mapping to CLBs


- ◆ Each LUT can go through a flip flop
  - So, these circuits map to the same number of Slices



CS/EE 3710

## Mapping to CLBs


- ◆ How about these?

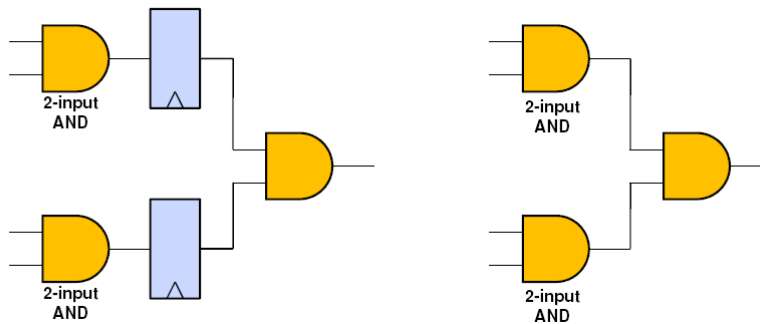

CS/EE 3710

## Mapping to CLBs

- ◆ How about these?

 

CS/EE 3710

## CLB Summary

- ◆ Each CLB = 4 slices
- ◆ Each slice contains
  - 2 LUT-4
    - LUT can be random logic, or 16x1bit RAM or SR
  - 2 flip flop
  - MUXs
  - Carry logic
- ◆ ISE reports how many slices you use
  - among lots of other things...

CS/EE 3710

# IO Blocks

- ◆ Connections to the outside world
  - Each pin can be configured a large number of ways
  - Different signaling voltages and drive currents

Single-Ended IOSTANDARD	V <sub>CC0</sub> Supply/Compatibility				
	1.2V	1.5V	1.8V	2.5V	3.3V
LVTTL	-	-	-	-	Input/Output
LVCMOS33	-	-	-	-	Input/Output
LVCMOS25	-	-	-	Input/Output	Input
LVCMOS18	-	-	Input/Output	Input	Input
LVCMOS15	-	Input/Output	Input	Input	Input
LVCMOS12	Input/Output	Input	Input	Input	Input
PCI33_3	-	-	-	-	Input/Output
PCI66_3	-	-	-	-	Input/Output

CS/EE 3710

# IO Blocks


- ◆ Connections to the outside world
  - Each pin can be configured a large number of ways
  - Different signaling voltages and drive currents

**NOTE! No 5v!**

IOSTANDARD	Output Drive Current (mA)					
	2	4	6	8	12	16
LVTTL	✓	✓	✓	✓	✓	✓
LVCMOS33	✓	✓	✓	✓	✓	✓
LVCMOS25	✓	✓	✓	✓	✓	-
LVCMOS18	✓	✓	✓	✓	-	-
LVCMOS15	✓	✓	✓	-	-	-
LVCMOS12	✓	-	-	-	-	-

Single-Ended IOSTANDARD	V <sub>CC0</sub> Supply/Compatibility				
	1.2V	1.5V	1.8V	2.5V	3.3V
LVTTL	-	-	-	-	Input/Output
LVCMOS33	-	-	-	-	Input/Output
LVCMOS25	-	-	-	Input/Output	Input
LVCMOS18	-	-	Input/Output	Input	Input
LVCMOS15	-	Input/Output	Input	Input	Input
LVCMOS12	Input/Output	Input	Input	Input	Input
PCI33_3	-	-	-	-	Input/Output
PCI66_3	-	-	-	-	Input/Output

# Inside an IOB

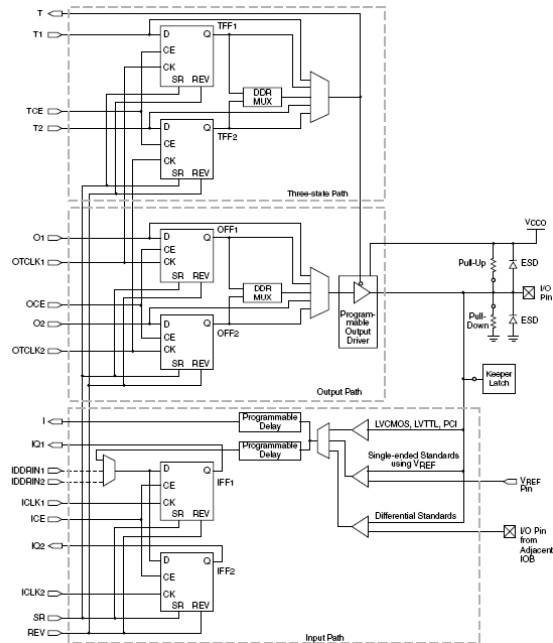

CS/EE 3710

# Interconnect

- ◆ Actually the most important part of the FPGA!
  - Consumes the most area on the die
  - Consumes the most power on the die
  - In most cases, wires limit the performance
- ◆ But, hardly mentioned in the datasheet
  - People are more impressed with logic

CS/EE 3710




# Interconnect

- ◆ RAM-programmable switches
  - 2,270,208 bits of configuration RAM!
  - Compare to 368,640 total bits of Block RAM
  - or 74,752 total bits of Distributed RAM (LUTs)
- ◆ Hierarchical organization
  - Many fast, short wires with small drive
  - Fewer longer wires with high drive
  - LOTS of work goes into picking just the right mix!

CS/EE 3710

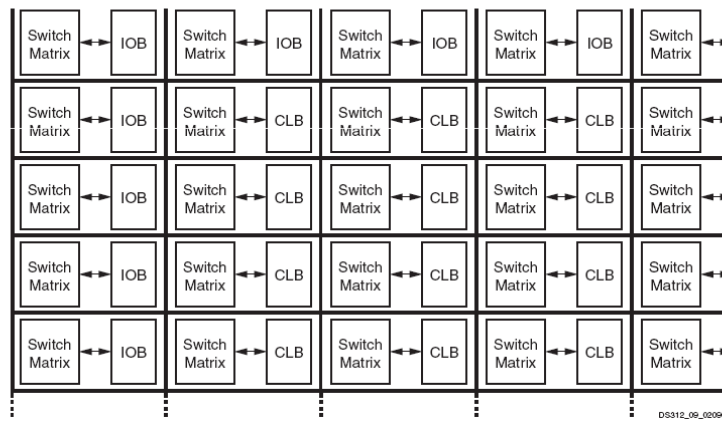
# Interconnect

- CLBs connect to 'switch matrix' which connects to the on-chip network
- Each switch matrix interconnects many different wires



# Interconnect


Four types of wires

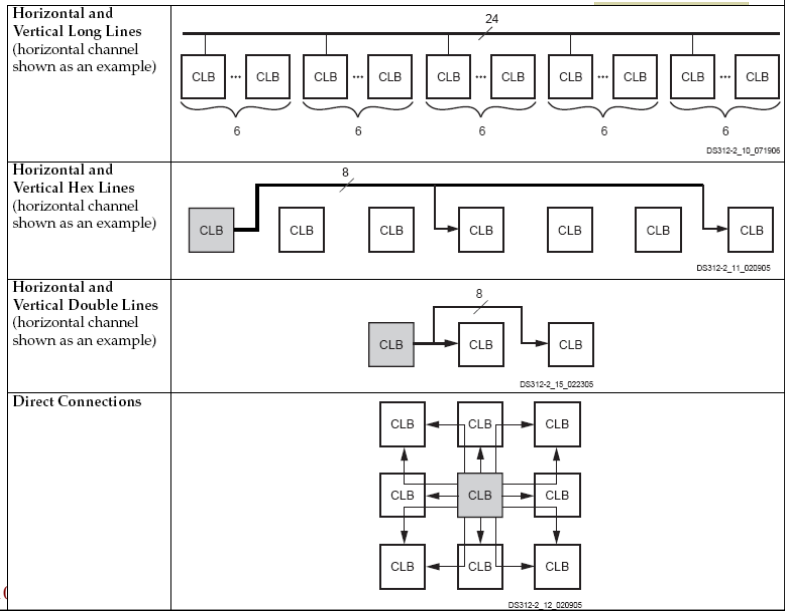

CS/EE 3710
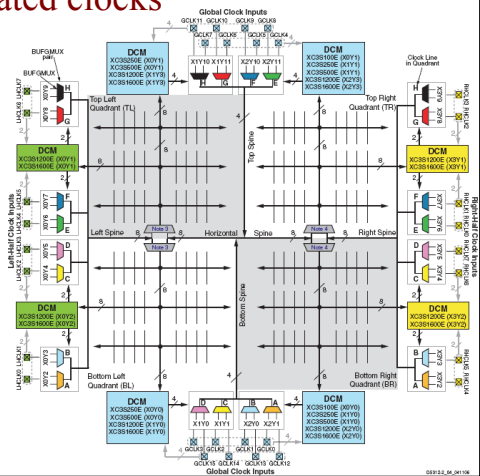
# Clock Routing

- ◆ Routed on a separate dedicated network
  - Another reason to avoid gated clocks
- ◆ Recursive “Fish bone” network that minimizes clock skew
- ◆ Clocks come from off-chip, or from a DCM



CS/EE 3710


# Spartan XC3E500S

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1200E	1200K	19,512	60	46	2,168	8,672	136K	504K	28	8	304	124
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

CS/EE 3710

# Block RAM

We've seen details of these already...

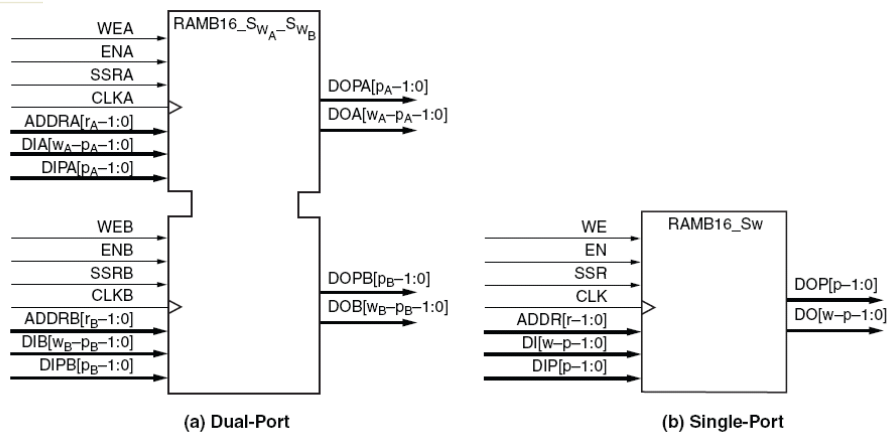

DS312-2\_03\_111105





# Distributed RAM

 
 


Figure 26: RAM16X1D Dual-Port Usage

CS/EE 3710

# Distributed RAM

```

parameter RAM_WIDTH = <ram_width>;
parameter RAM_ADDR_BITS = <ram_addr_bits>;

reg [RAM_WIDTH-1:0] <ram_name> [(2**RAM_ADDR_BITS)-1:0];

wire [RAM_WIDTH-1:0] <output_data>;

<reg_or_wire> [RAM_ADDR_BITS-1:0] <read_address>, <write_address>;
<reg_or_wire> [RAM_WIDTH-1:0] <input_data>;

always @ (posedge <clock>)
    if (<write_enable>)
        <ram_name>[<write_address>] <= <input_data>;

assign <output_data> = <ram_name>[<read_address>];
    
```

## Dual-Port Distributed RAM

CS/EE 3710

## Distributed RAM

```
RAM16X1D #(
    .INIT(16'h0000) // Initial contents of RAM
) RAM16X1D_inst (
    .DPO(DPO),      // Read-only 1-bit data output for DPRA
    .SPO(SPO),      // R/W 1-bit data output for A0-A3
    .A0(A0),        // R/W address[0] input bit
    .A1(A1),        // R/W address[1] input bit
    .A2(A2),        // R/W address[2] input bit
    .A3(A3),        // R/W address[3] input bit
    .D(D),          // Write 1-bit data input
    .DPRA0(DPRA0), // Read address[0] input bit
    .DPRA1(DPRA1), // Read address[1] input bit
    .DPRA2(DPRA2), // Read address[2] input bit
    .DPRA3(DPRA3), // Read address[3] input bit
    .WCLK(WCLK),   // Write clock input
    .WE(WE)        // Write enable input
);
```

### Dual-Port Distributed RAM

CS/EE 3710

## Digital Clock Manager (DCM)

DCMs integrate advanced clocking capabilities directly into the FPGA's global clock distribution network. Consequently, DCMs solve a variety of common clocking issues, especially in high-performance, high-frequency applications:


- **Eliminate Clock Skew**, either within the device or to external components, to improve overall system performance and to eliminate clock distribution delays.
- **Phase Shift** a clock signal, either by a fixed fraction of a clock period or by incremental amounts.
- **Multiply or Divide an Incoming Clock Frequency** or synthesize a completely new frequency by a mixture of clock multiplication and division.
- **Condition a Clock**, ensuring a clean output clock with a 50% duty cycle.
- **Mirror, Forward, or Rebuffer a Clock Signal**, often to deskew and convert the incoming clock signal to a different I/O standard—for example, forwarding and converting an incoming LVTTTL clock to LVDS.
- **Any or all the above functions, simultaneously.**

CS/EE 3710

# Digital Clock Manager (DCM)



 
a. Global Buffer Inputs and Clock Buffers Drive a Low-Skew Global Network in the FPGA



b. A Digital Clock Manager (DCM) Inserts Directly into the Global Clock Path


CS/EE 3710

# Digital Clock Manager (DCM)

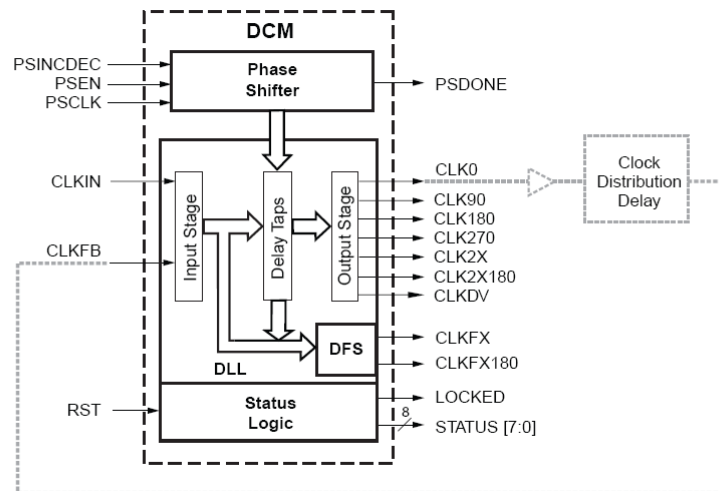




# Clock Skew

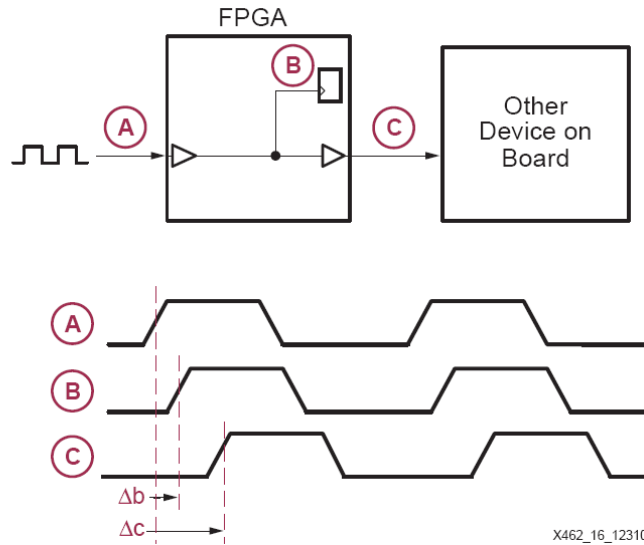

# Clock Skew

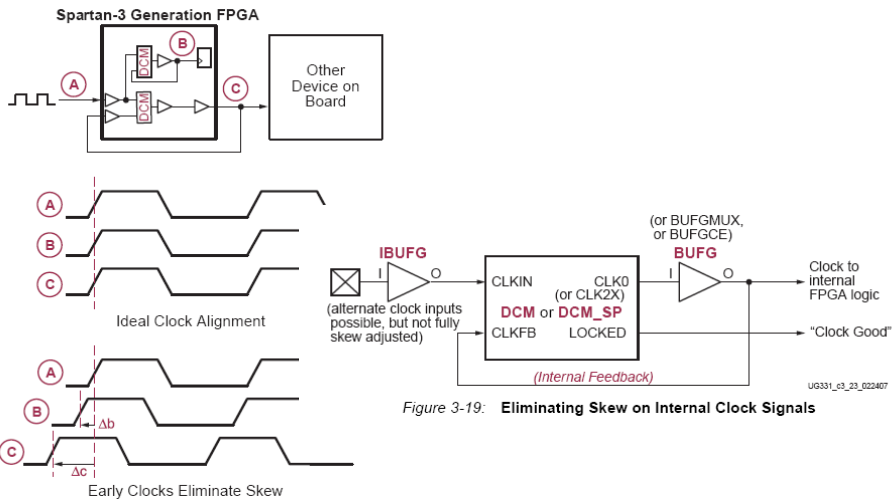

# Multipliers

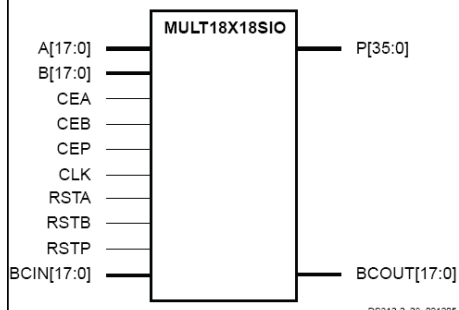


Figure 11-1: MULT18X18SIO Primitive

 


Figure 11-3: Principle Ports and Functions of Dedicated Multiplier Blocks

CS/EE 3710

# Multipliers

```
module mult18x18sio(a,b,clk,prod);  
    input [7:0] a;  
    input [7:0] b;  
    input clk;  
    output [15:0] prod;  
    reg [15:0] prod;  
    always @(posedge clk) prod <= a*b;  
endmodule
```


CS/EE 3710

# Synthesis Output (mips example)

Device Utilization Summary			
Logic Utilization	Used	Available	Utilization
Number of Slice Flip Flops	79	9,312	1%
Number of 4 input LUTs	193	9,312	2%
<b>Logic Distribution</b>			
Number of occupied Slices	123	4,656	2%
Number of Slices containing only related logic	123	123	100%
Number of Slices containing unrelated logic	0	123	0%
<b>Total Number of 4 input LUTs</b>	<b>193</b>	<b>9,312</b>	<b>2%</b>
Number used as logic	161		
Number used for Dual Port RAMs	32		
Number of bonded IOBs			
Number of bonded	19	232	8%
Number of RAMB16s	1	20	5%
Number of BUFGMUXs	1	24	4%

CS/EE 3710


# Synthesis Output (mips example)

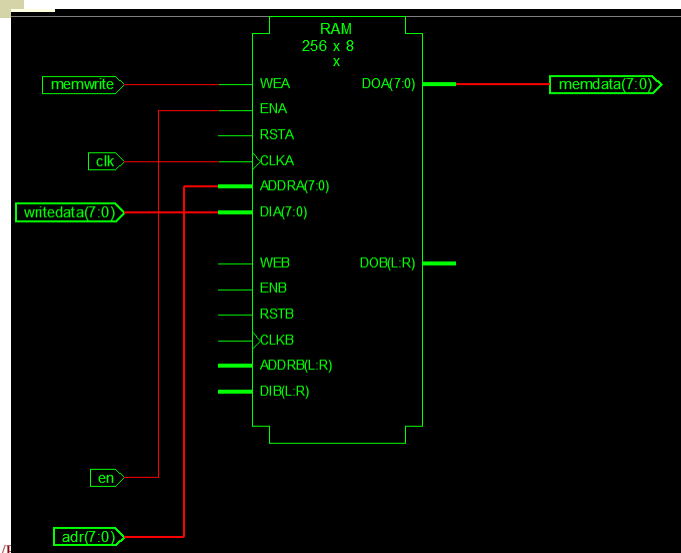

CS/EE 3710




## Synthesis Output (mips example)

 


CS/EE 3710

## Implement Output (mips example)

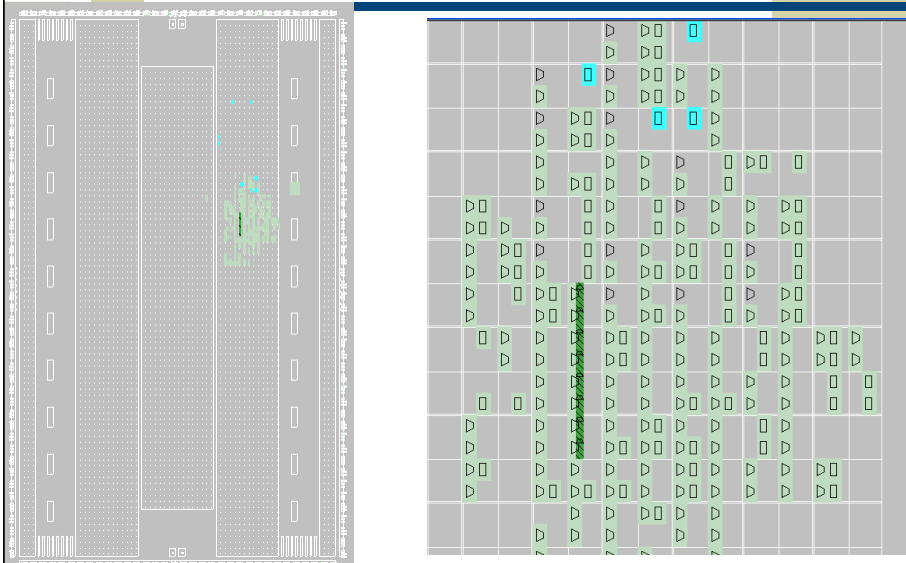


CS/EE 3710


## Implement Output (mips example)

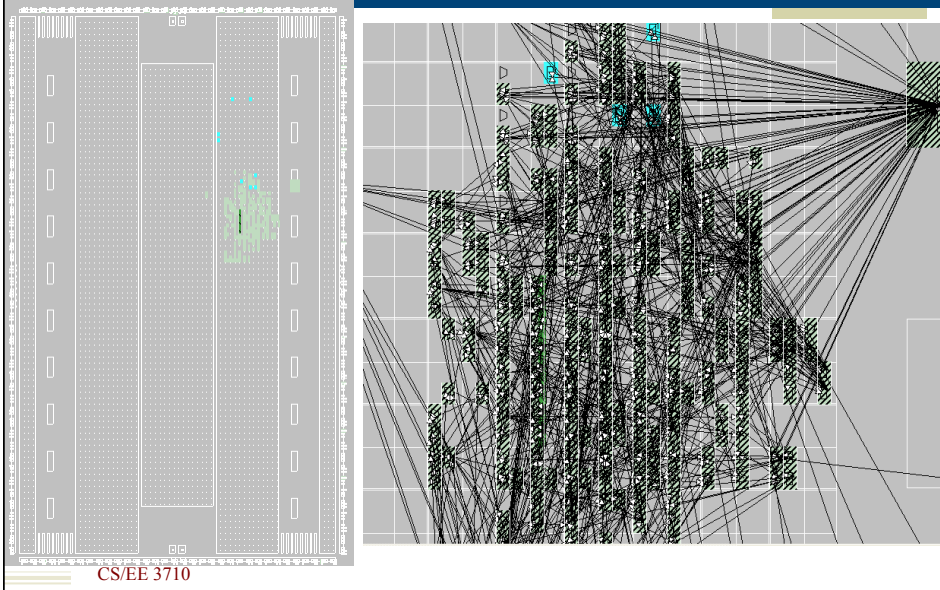


## Implement Output (mips example)

 


## Implement Output (mips example)

 


## Implement Output (mips example)

 

## Implement Output (mips example)

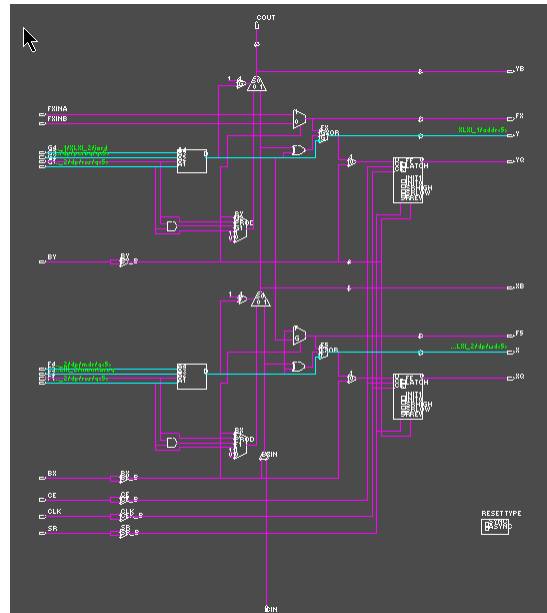

## Implement Output (mips example)

 



## Conclusion

- ◆ FPGAs are complex beasts!
  - Made to be very general and flexible
- ◆ ASIC vs. FPGA?
  - Rule of thumb, FPGA about 5 times slower clock than ASIC
  - FPGAs consume more power
  - FPGAs are bigger for the same function
  - ASICs are *much* more expensive to develop
    - NRE – Non-Recurring Engineering

CS/EE 3710

## ASIC vs. FPGA

FPGA & ASIC Design Advantages	
FPGA Design Advantages	ASIC Design Advantages
<b>Faster time-to-market</b> - no layout, masks or other manufacturing steps are needed	<b>Full custom capability</b> - for design since device is manufactured to design specs
<b>No upfront NRE</b> (non recurring expenses) - costs typically associated with an ASIC design	<b>Lower unit costs</b> - for very high volume designs
<b>Simpler design cycle</b> - due to software that handles much of the routing, placement, and timing	<b>Smaller form factor</b> - since device is manufactured to design specs
<b>More predictable project cycle</b> - due to elimination of potential re-spins, wafer capacities, etc.	<b>Higher raw internal clock speeds</b>
<b>Field reprogrammability</b> - a new bitstream can be uploaded remotely	

CS/EE 3710