

## INTERFACING WITH OTHER CHIPS


Examples of three LED driver chips

### Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino

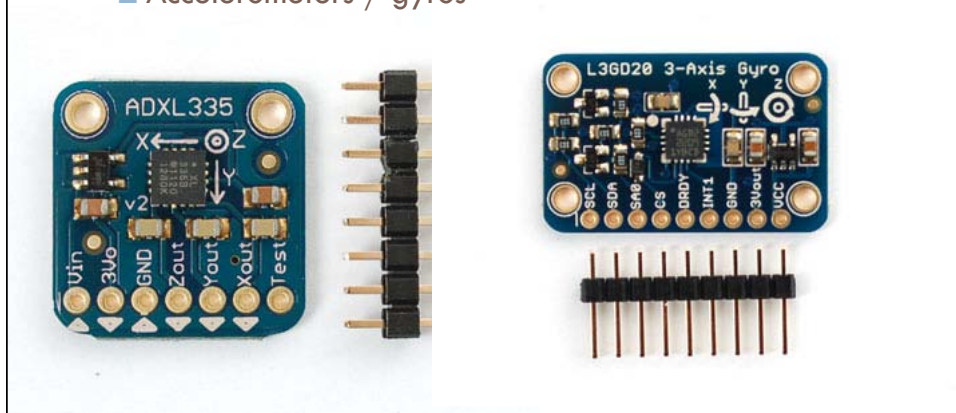
## Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ Accelerometers / gyros



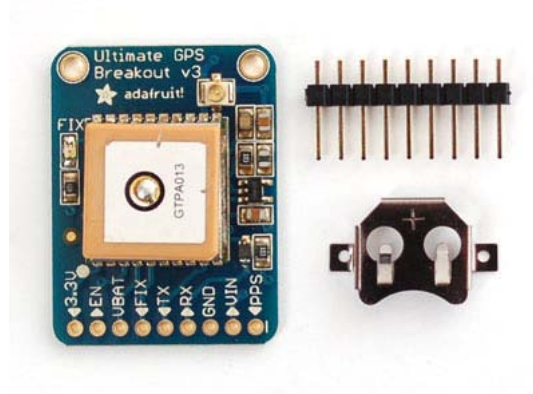
## Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ Accelerometers / gyros
  - ▣ GPS


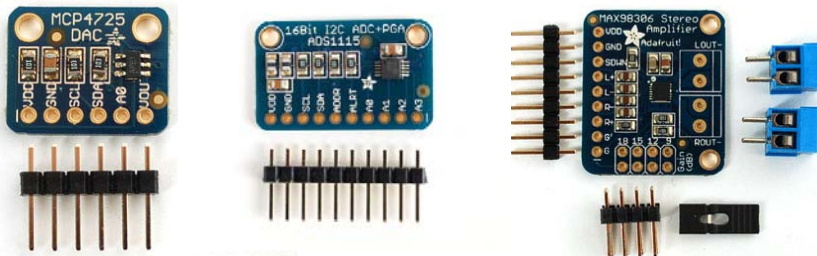
## Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ Accelerometers / gyros
  - ▣ GPS
  - ▣ audio – amps, external ADC/DAC, etc.





## Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ Accelerometers / gyros
  - ▣ GPS
  - ▣ audio – amps, external ADC/DAC, etc.
  - ▣ displays – FVD, TFT, etc.



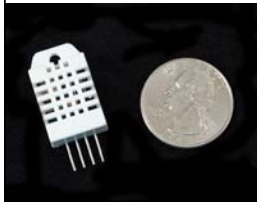
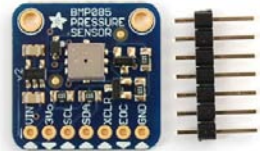
## Why Add Other Chips?

- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ Accelerometers / gyros
  - ▣ GPS
  - ▣ audio – amps, external ADC/DAC
  - ▣ displays – FVD, TFT, etc.
  - ▣ Environmental sensors – temp, humidity, barometer, etc.


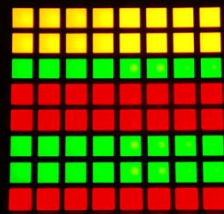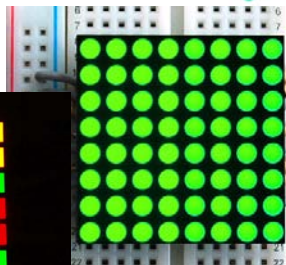
## Why Add Other Chips?


- Lots of cool chips out there that add functionality beyond a basic Arduino
  - ▣ LEDs – lots of 'em



## Why Add Other Chips?


- Driving External LEDs
  - ▣ From an Arduino you can drive 14 LEDs directly from the digital outs – what if you want more?
  - ▣ Use external LED-driver chip
  - ▣ Send data on which LEDs to turn on and of to that chip
  - ▣ Let it keep track of the LEDs while you do other things

## Leo Villareal

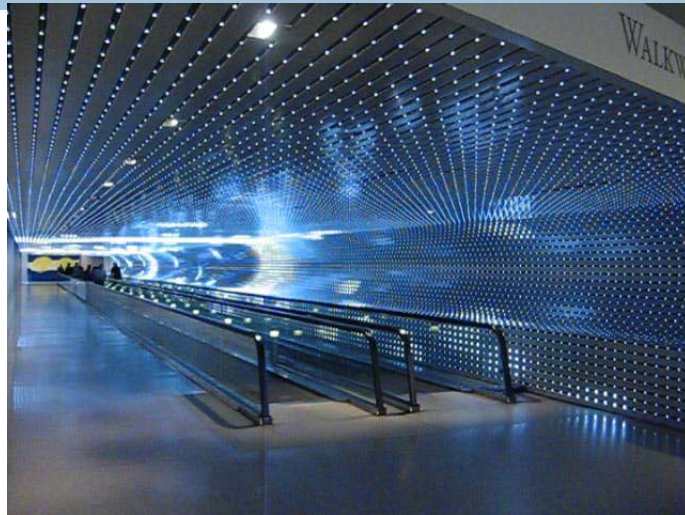

National Gallery of Art

# Leo Villareal

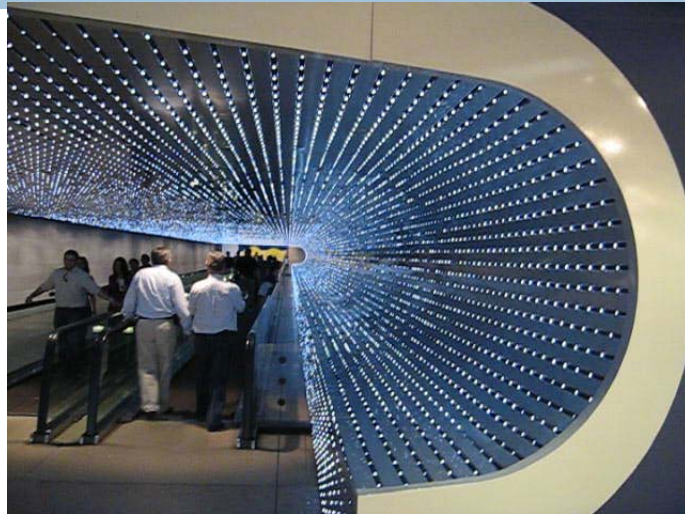

National Gallery of Art

# Leo Villareal







## Jenny Holzer

Cylinder of LED strips  
28 feet tall  
4 feet in diameter

Smithsonian






## CMU Campus






## Aristarkh Chernyshev

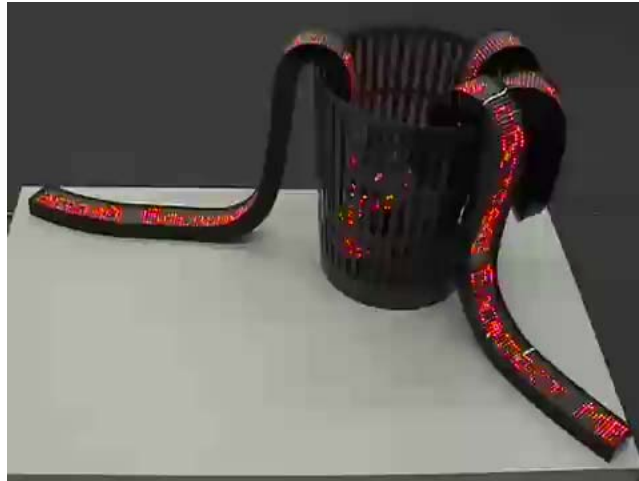


## Jim Campbell (1956 - )



## Jim Campbell (1956 -)

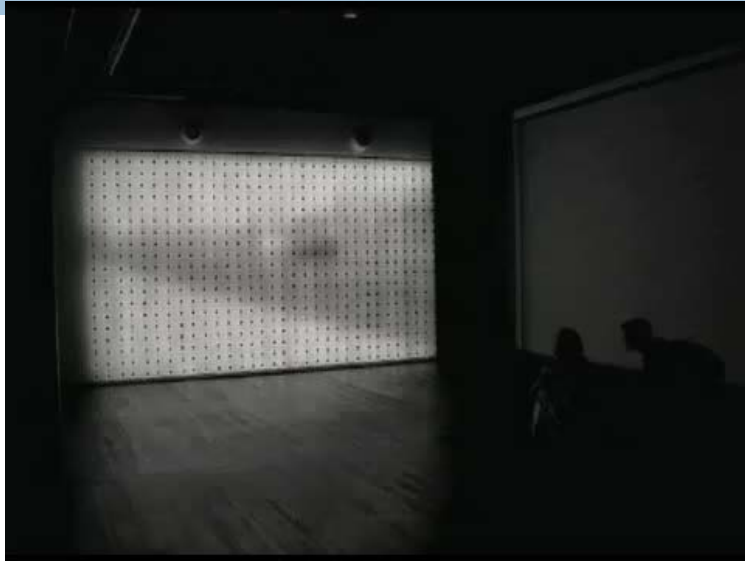


## Jim Campbell (1956 -)

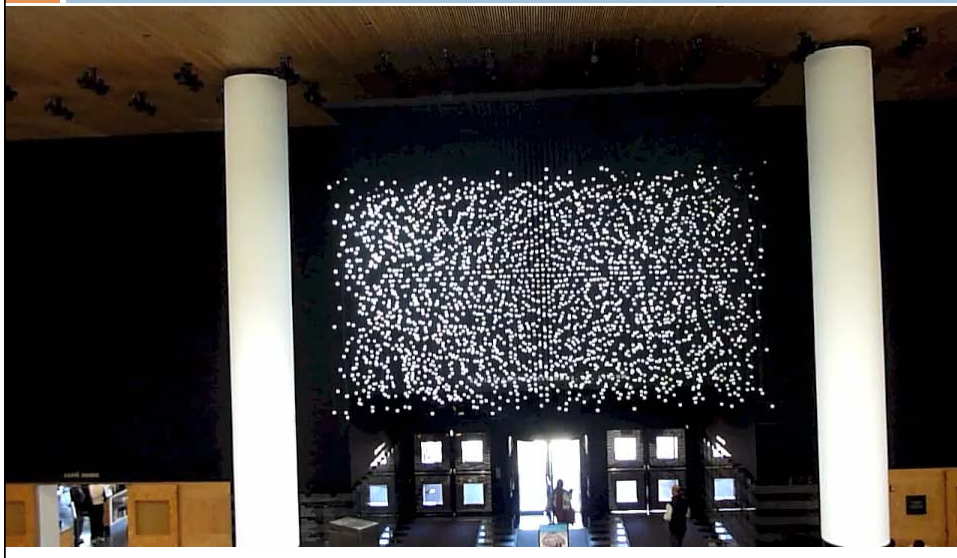

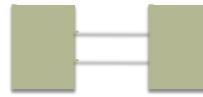
## Communication Styles

- **Parallel** = multiple wires in parallel
- **Serial** = send data one at a time on one wire
  - ▣ In practice you usually need two wires: one for the data, and one to say when to look at the data (usually called Clock)
- So, serial communication takes more time, but uses fewer wires



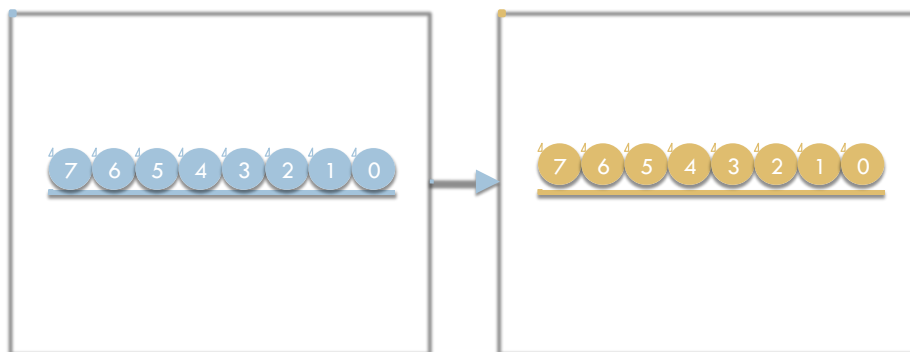
## Shifting

- Shifting is the process of sending out a set of bits one at a time



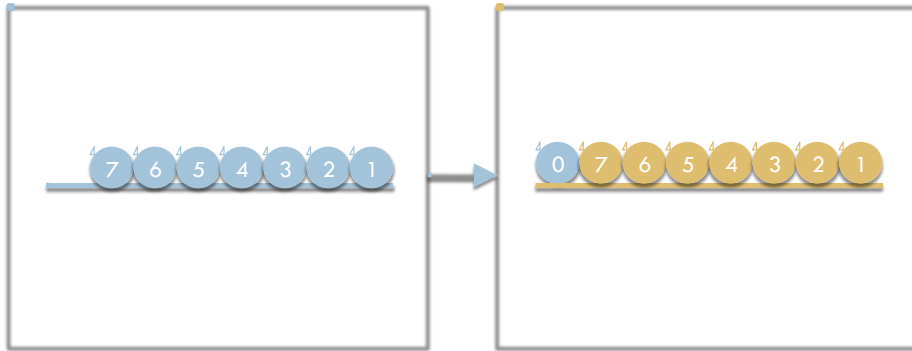
## Shifting

- Shifting is the process of sending out a set of bits one at a time



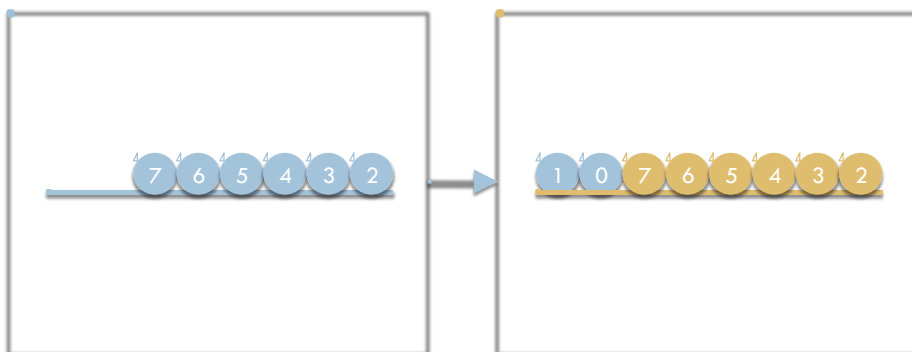
## Shifting

- Shifting is the process of sending out a set of bits one at a time



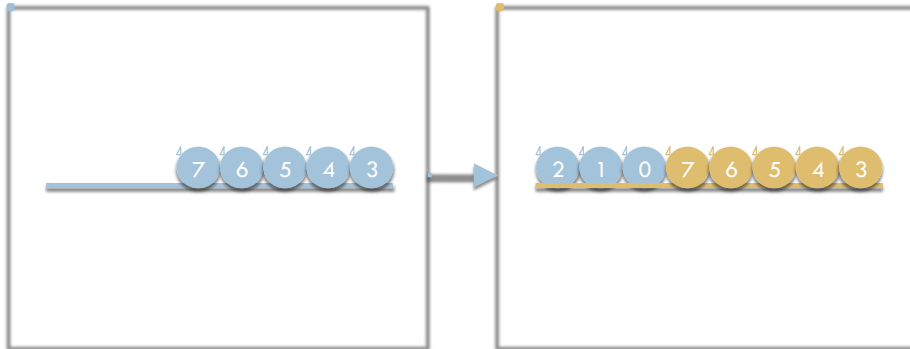
## Shifting

- Shifting is the process of sending out a set of bits one at a time


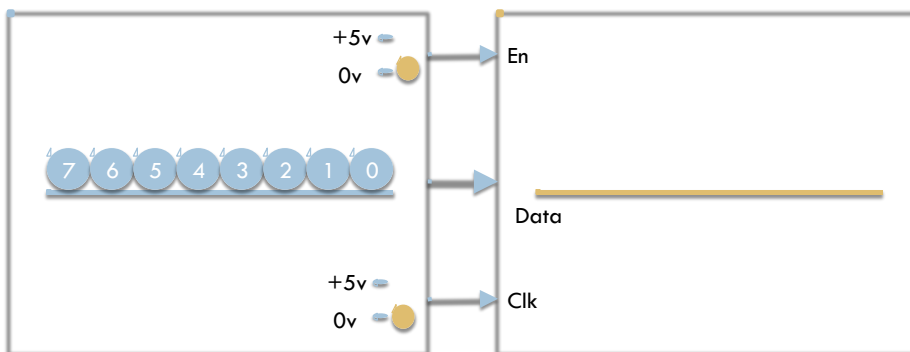
## Shifting

- There are a couple other control signals too...





## Overview

- There are a number of different protocols used for inter-chip communication (Arduino to external chip...)
  - ▣ Serial output – simplest protocol
    - Also called SPI – Serial Peripheral Interface
    - CLK/Data/En, unidirectional
    - Example: STP08DP05 8-bit LED driver

## Overview

- There are a number of different protocols used for inter-chip communication (Arduino to external chip...)
  - ▣ Serial output – SPI
    - Example: STP08DP05 8-bit LED driver
  - ▣ SPI with more complex operation
    - Send data with SPI, both commands and data
    - Example: MAX 7219 8-digit LED display driver
    - Also LED strips

## Overview


- There are a number of different protocols used for inter-chip communication (Arduino to external chip...)
  - Serial output – SPI
    - Example: STP08DP05 8-bit LED driver
  - SPI with more complex operation
    - Example: MAX 7219 8-digit LED display driver
    - LED strips
  - I<sup>2</sup>C/TWI – two-wire interface – more complex
    - CLK/Data - bidirectional
    - Example: Wii Nunchuck

## Overview

- There are a number of different protocols used for inter-chip communication (Arduino to external chip...)
  - Serial output – SPI
    - Example: STP08DP05 8-bit LED driver
  - SPI with more complex operation
    - Example: MAX 7219 8-digit LED display driver
  - I<sup>2</sup>C/TWI – two-wire interface – more complex
    - Example: Wii Nunchuck
  - Custom protocols – potentially complex
    - Example: TLC5940 16-bit PWM LED driver

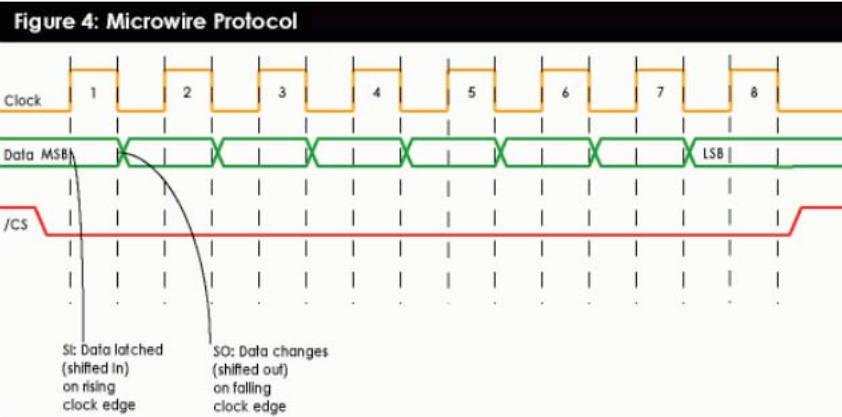
## SPI Serial Output

- Two pins: Clk and Data
  - New data presented at Data pin on every clock
  - Looks like a shift register


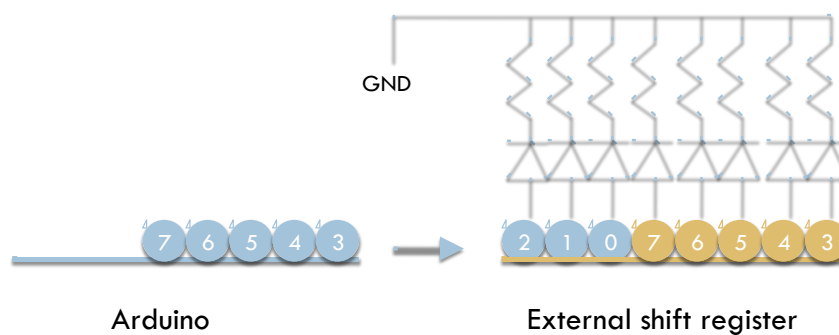
## Example: Shift Register

- Simply connect LEDs to the outputs of the shift register
- The only problem is that the LED pattern changes while you're shifting it in...




## Shifter with Output Latch

- One solution is to save the current outputs while you're shifting in the new ones
  - ▣ This is an “output latch”
  - ▣ Shift in new stuff “underneath” the bits that are being displayed
  - ▣ Then, all at once, swap the new bits for the old bits

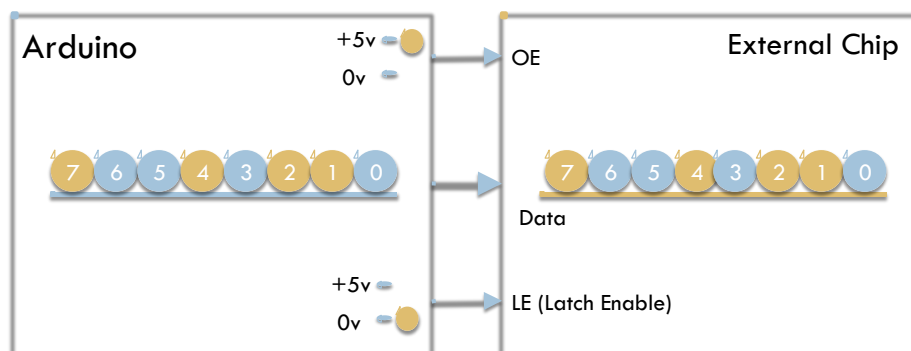
## Shifting w/Latch

- latch when LE goes high
- Outputs enabled when OE is low




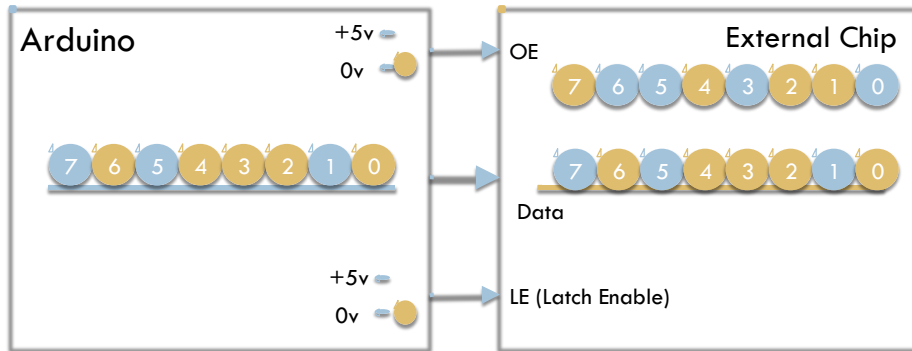
## Shifting w/Latch

- latch when LE goes high
- Outputs enabled when OE is low


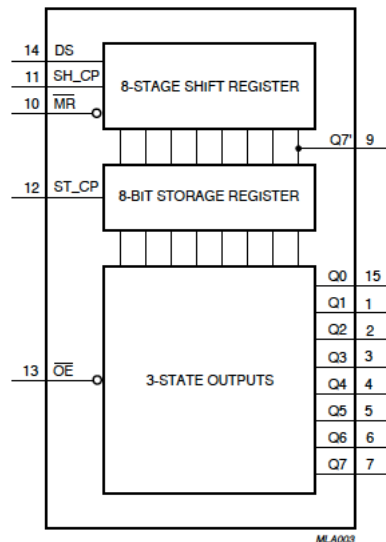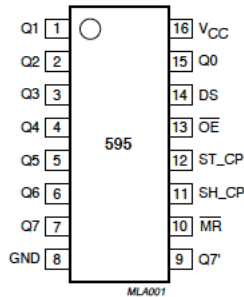
## Example: 74HC595

- This is a shift register
  - with an output latch
- You can save the previous values while shifting in new ones
- **BUT – need separate current-limiting resistor for each LED!**






## Example: STP08DP05

- Just like the 74HC595 – a shift register with a separate output latch
- ALSO – **constant-current outputs for the LEDs**
  - ▣ That means the outputs limit the current for you
  - ▣ You set the output current with a single resistor for all 8 outputs
  - ▣ Only one resistor for 8 LEDs!

## Example: STP08DP05

Figure 2. Normal mode - block diagram

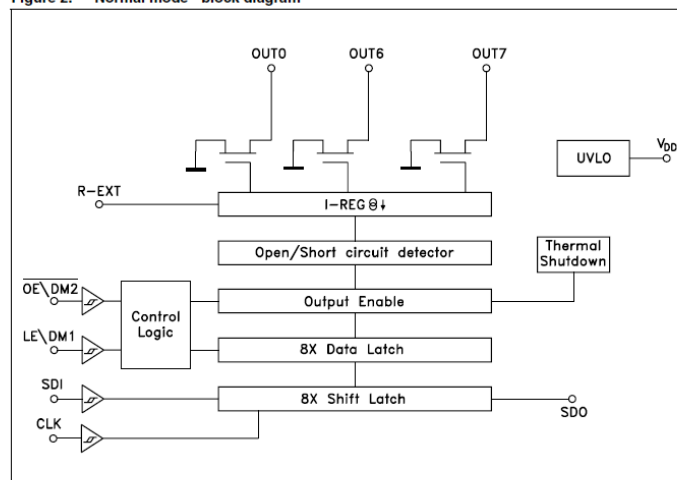

SDI/CLK shifts data into the 8-bit shift-register


LE moves data to the “data latch” so that it can be seen on the output

OE controls whether the data is enabled to drive the outputs

R-EXT sets the current limit for all outputs

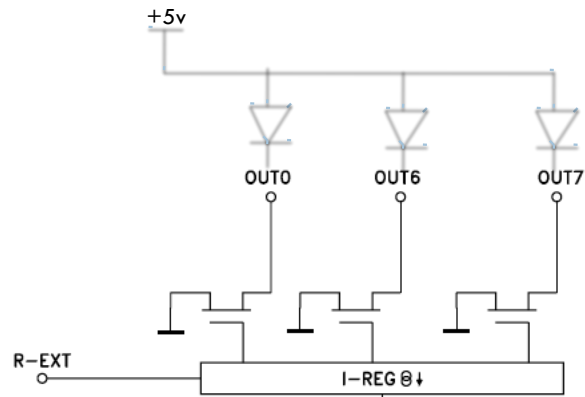
## Constant Current Source

- Note that the constant current source only pulls to ground
  - ▣ So – LEDs connect to vdd...



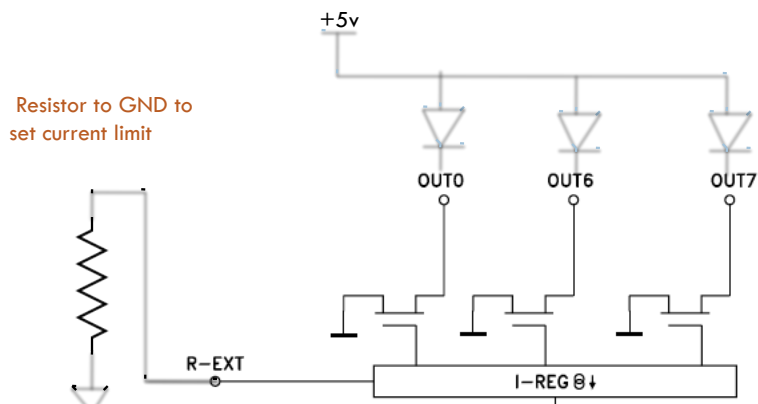
## Constant Current Source

- Note that the constant current source only pulls to ground
  - ▣ So – LEDs connect to vdd...



## Example: STP08DP05

Figure 7. Timing diagram - normal mode

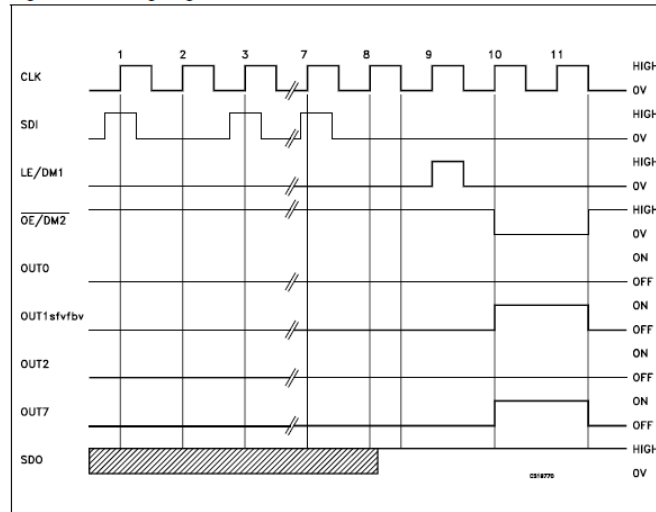

Timing diagram shows shifting data in, one bit per clock

Data is transferred to output register on a high LE

Data shows up only when OE is low

This means you can dim all 8 LEDs using PWM on the OE signal

## Arduino Code

- Arduino has a built-in function to shift data out for devices like this

### Syntax

```
shiftOut(dataPin, clockPin, bitOrder, value)
```

### Parameters

dataPin: the pin on which to output each bit (*int*)

clockPin: the pin to toggle once the **dataPin** has been set to the correct value (*int*)

bitOrder: which order to shift out the bits; either **MSBFIRST** or **LSBFIRST**.  
(Most Significant Bit First, or, Least Significant Bit First)

value: the data to shift out. (*byte*)

### Returns

None

## Internal Arduino Code for shiftOut()

```

void shiftOut(uint8_t dataPin, uint8_t clockPin, uint8_t bitOrder, byte val)
{
  int i;
  for (i = 0; i < 8; i++) {
    if (bitOrder == LSBFIRST)
      digitalWrite(dataPin, !(val & (1 << i)));
    else
      digitalWrite(dataPin, !(val & (1 << (7 - i))));

    digitalWrite(clockPin, HIGH);
    digitalWrite(clockPin, LOW);
  }
}

```

## User Arduino Code (STP08DP05)

```

const int latchPin = 8; //Pin connected to LE of STP08DP05
const int clockPin = 12; //Pin connected to CLK of STP08DP05
const int dataPin = 11; //Pin connected to SDI of STP08DP05
const int OEPin = 10; //Pin connected to OEbar of STP08DP05

void setup() { //set pins to output because they are addressed in the main loop
  pinMode(latchPin, OUTPUT);
  pinMode(clockPin, OUTPUT);
  pinMode(dataPin, OUTPUT);
  pinMode(OEPin, OUTPUT);}
void loop() { //count up routine
  for (int i = 0; i < 256; i++) { // count i from 0 to 255 (00000000 to 11111111)

    //ground latchPin and hold low for as long as you are transmitting, OE pin is high...
    digitalWrite(latchPin, LOW); digitalWrite(OEPin, HIGH);

    shiftOut(dataPin, clockPin, LSBFIRST, i); // shift out the value of i

    //return the latch pin high to transfer data to output latch, OE low to light the LEDs
    digitalWrite(latchPin, HIGH); digitalWrite(OEPin, LOW);
  }
  delay(1000); }}

```

# Chaining Multiple Chips

Figure 2. Normal mode - block diagram


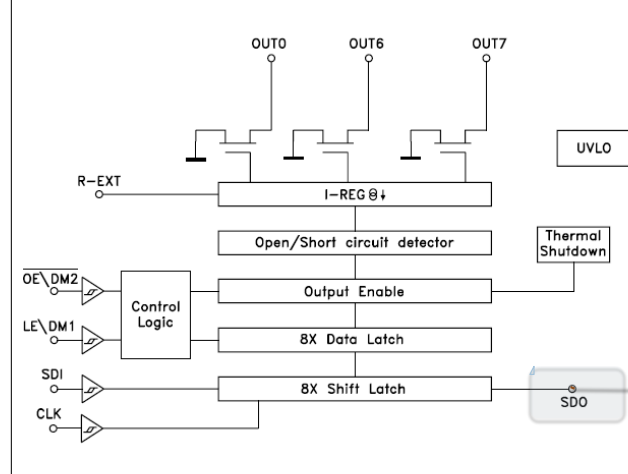


Figure 2. Normal mode - block diagram

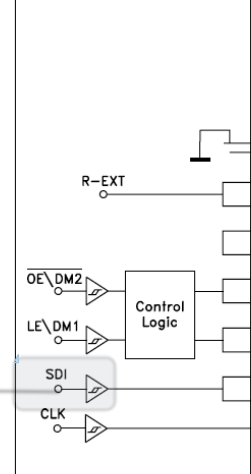

# Choosing a Resistor

- I chose a 2k ohm resistor for around 10ma

Figure 11. Output current- $R_{EXT}$  resistor

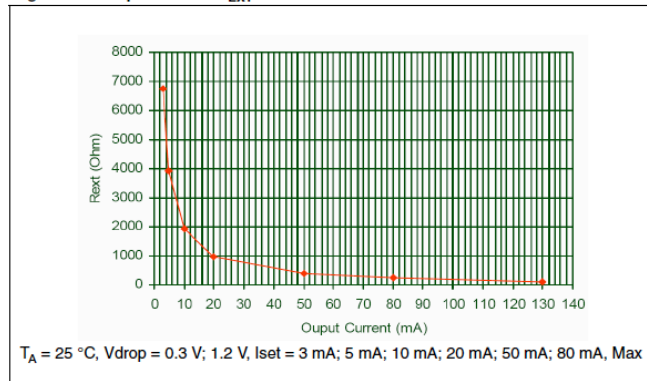


Table 10. Output current- $R_{EXT}$  resistor

Output current (mA)	3	5	10	20	50	80	130
$R_{ext} (\Omega)$	6740	3930	1913	963	386	241	124

Maximum output current capabilities setting was 130 mA applying an  $R_{ext} = 124 \Omega$




## STP08DP05 Summary

- Easy chip to use
  - ▣ Use ShiftOut(...) to shift data to the chip
  - ▣ Can chain many together to drive lots of LEDs
- Just four wires from Arduino to external chip drives 8 LEDs (per chip – you can also chain)
  - ▣ Clk and Data used to shiftOut() the data
  - ▣ LE goes high to capture the data
  - ▣ OE goes low to make the data appear (or for PWM)
- Constant-current drivers so only one resistor per chip
  - ▣ Simple on or off for each LED


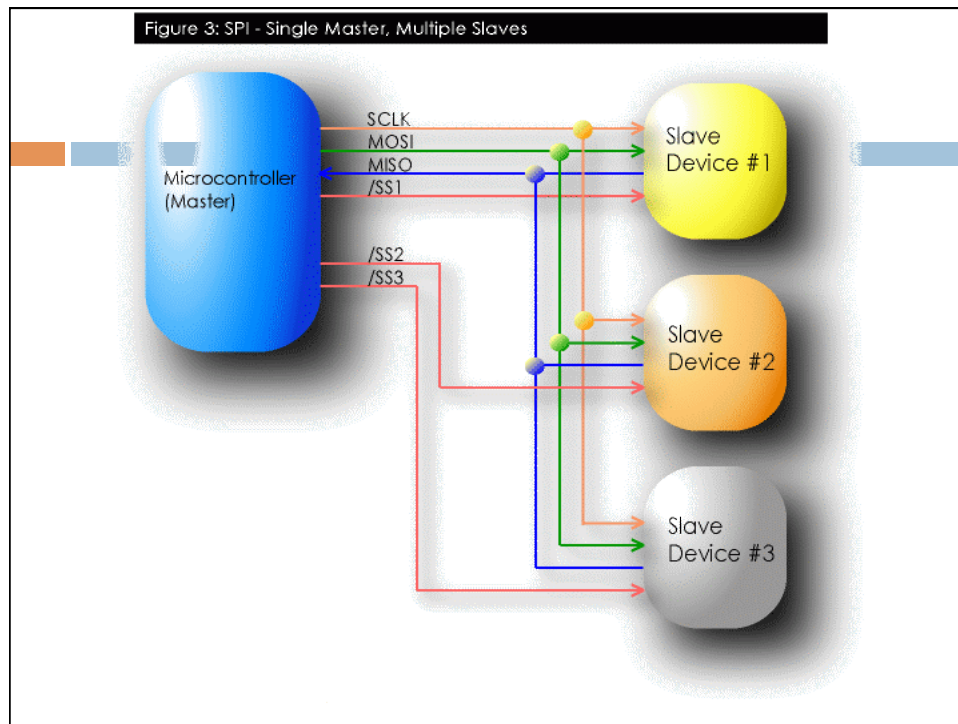
## SPI Interface

- Serial Peripheral Interface
  - ▣ Generalized version of previous example
  - ▣ “official” version has bidirectional data – you can read back data from the other device at the same time as you’re sending
  - ▣ But, you can ignore that and use the same ShiftOut function if you like



## Example: MAX 7219

- Display driver for 8-digits of 7-segment numbers
  - ▣ Can also be used for 8x8 array of LEDs
    - (i.e. 64 individual LEDs)
- Drives common-cathode LED digits or LED matrix
  - ▣ Cycles between each of 8 digits (or matrix rows) fast enough so they all look ON
- SPI interface
  - ▣ Slightly complicated command/data interface
  - ▣ Send address of internal register followed by data
  - ▣ Each SPI communication is 16 bits
  - ▣ Luckily, there's an Arduino library for the chip

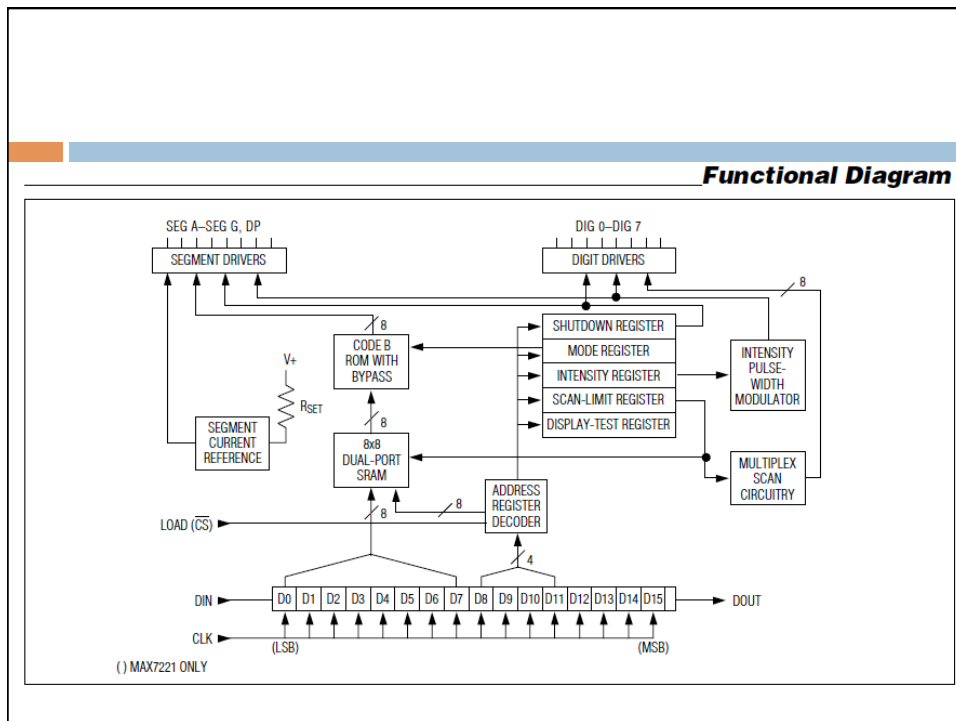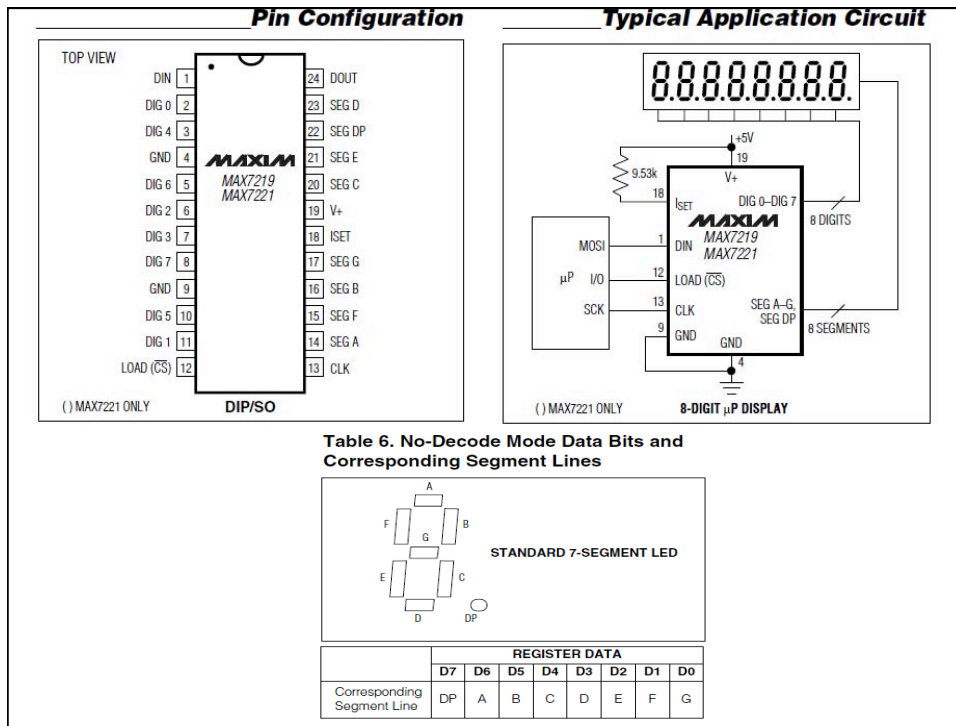

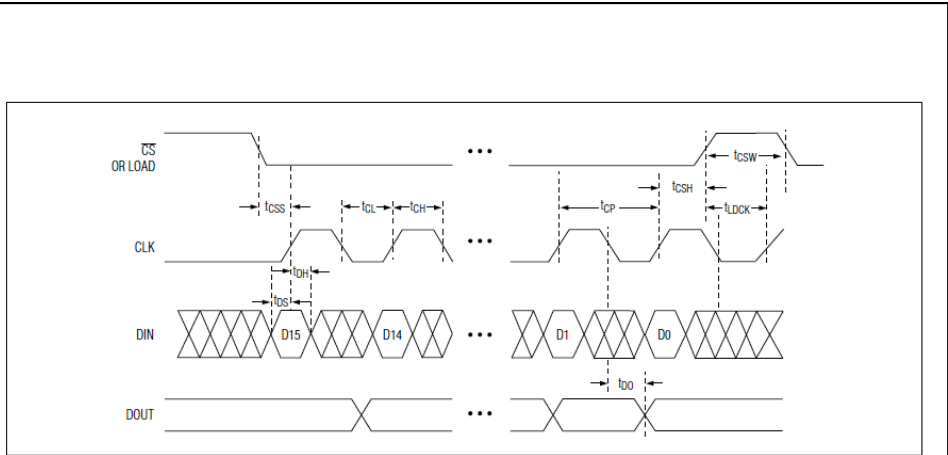



Figure 1. Timing Diagram

Table 1. Serial-Data Format (16 Bits)

D15	D14	D13	D12	D11	D10	D9	D8	D7	D6	D5	D4	D3	D2	D1	D0
X	X	X	X	ADDRESS				MSB	DATA						LSB

Table 2. Register Address Map

REGISTER	ADDRESS					HEX CODE
	D15-D12	D11	D10	D9	D8	
No-Op	X	0	0	0	0	0xX0
Digit 0	X	0	0	0	1	0xX1
Digit 1	X	0	0	1	0	0xX2
Digit 2	X	0	0	1	1	0xX3
Digit 3	X	0	1	0	0	0xX4
Digit 4	X	0	1	0	1	0xX5
Digit 5	X	0	1	1	0	0xX6
Digit 6	X	0	1	1	1	0xX7
Digit 7	X	1	0	0	0	0xX8
Decode Mode	X	1	0	0	1	0xX9
Intensity	X	1	0	1	0	0xXA
Scan Limit	X	1	0	1	1	0xXB
Shutdown	X	1	1	0	0	0xXC
Display Test	X	1	1	1	1	0xFF

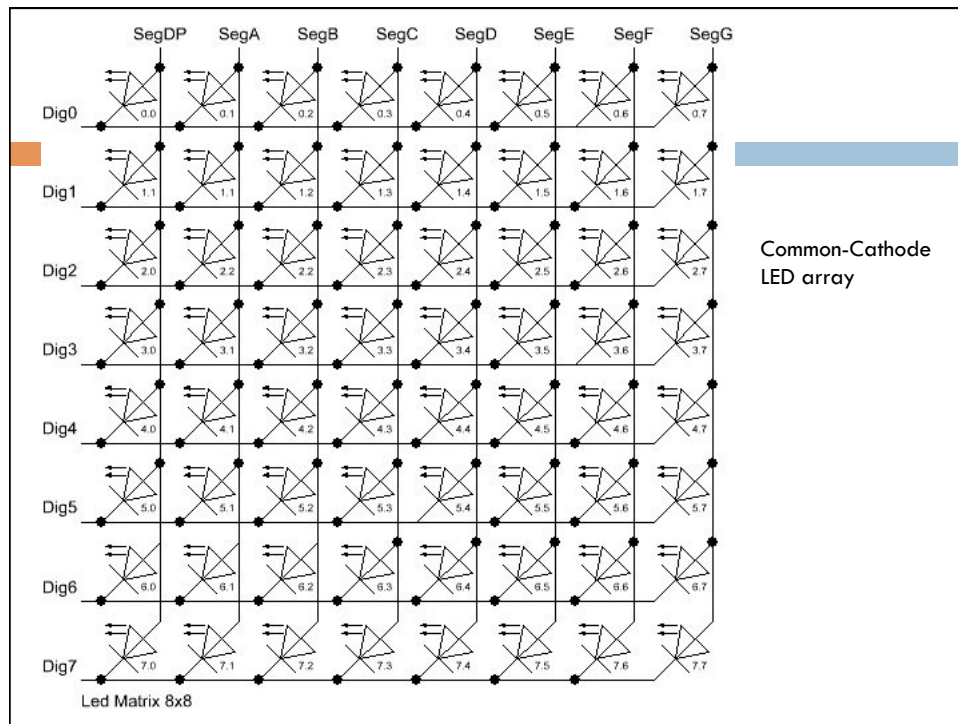

## MAX 7219

- On the one hand – just like STP08DP05
- On the other hand, more complex internal structure
  - ▣ Each SPI transfer needs to be 16 bits – address/data
- (at least) Two Arduino libraries available
  - ▣ Matrix – built-in to Arduino environment
  - ▣ LedControl – download from Playground – more complex control



## LedControl Library

- Support for more than one MAX 7219
- Support for numbers and letters on 7-segment displays
- Support for rows and columns in an 8x8 matrix

## LedControl Library

```

/* We start by including the library */
#include "LedControl.h"

/* Make a new instance of an LedControl object
 * Params :
 * int dataPin  The pin on the Arduino where data gets shifted out (Din on MAX)
 * int clockPin  The pin for the clock (CLK on MAX)
 * int csPin    The pin for enabling the device (LD/CS on MAX)
 * int numDevices The maximum number of devices that can be controlled
 */
LedControl lc1 = LedControl(12,11,10,1);

```

## LedControl Library

```
void clearDisplay(int addr);
void setLed(int addr, int row, int col, boolean state);
void setRow(int addr, int row, byte value);
void setColumn(int addr, int col, byte value);
void setDigit(int addr, int digit, byte value, boolean dp);
void setChar(int addr, int digit, char value, boolean dp);
```

```
/*
 * Display a character on a 7-Segment display.
 * There are only a few characters that make sense here :
 * '0','1','2','3','4','5','6','7','8','9','0',
 * 'A','b','c','d','E','F','H','L','P',
 * ' ','-','_','.'
 */
```

## LedControl Library

```
//include this file so we can write down a byte in binary encoding
#include <binary.h>

//now setting the leds in the sixth column on the first device is easy
lc.setColumn(0,5,B00001111);

//now setting the leds from the third row on the first device is easy
lc.setRow(0,2,B10110000);

//switch on the led in the 3'rd row 8'th column
//and remember that indices start at 0!
lc.setLed(0,2,7,true);
//Led at row 0 second from left too
lc.setLed(0,0,1,false);
```

## LedControl Library

```

void writeArduinoOnMatrix() {
  /* here is the data for the characters */
  byte a[5]={B01111110,B10001000,B10001000,B10001000,B01111110};
  byte r[5]={B00111110,B00010000,B00100000,B00100000,B00010000};
  byte d[5]={B00011100,B00100010,B00100010,B00010010,B11111110};
  byte u[5]={B00111100,B00000010,B00000010,B00000100,B00111110};
  byte i[5]={B00000000,B00100010,B10111110,B00000010,B00000000};
  byte n[5]={B00111110,B00010000,B00100000,B00100000,B00011110};
  byte o[5]={B00011100,B00100010,B00100010,B00100010,B00011100};

  /* now display them one by one with a small delay */
  lc.setRow(0,0,a[0]);
  lc.setRow(0,1,a[1]);
  lc.setRow(0,2,a[2]);
  lc.setRow(0,3,a[3]);
  lc.setRow(0,4,a[4]);
  delay(delaytime);
  lc.setRow(0,0,r[0]);
  lc.setRow(0,1,r[1]);
  lc.setRow(0,2,r[2]);
  lc.setRow(0,3,r[3]);
  lc.setRow(0,4,r[4]);
  delay(delaytime);
}
    
```

## MAX 7219 – Current Setting Resistor

- This resistor goes to Vdd, NOT GND!
- Sets current for each segment (LED)


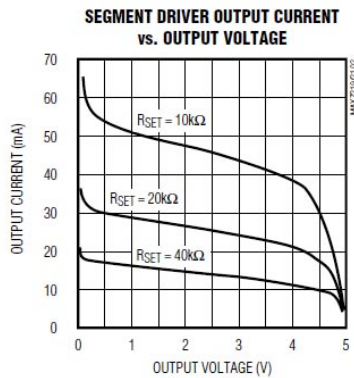


Table 11. RSET vs. Segment Current and LED Forward Voltage


ISEG (mA)	VLED (V)				
	1.5	2.0	2.5	3.0	3.5
40	12.2	11.8	11.0	10.6	9.69
30	17.8	17.1	15.8	15.0	14.0
20	29.8	28.0	25.9	24.5	22.6
10	66.7	63.7	59.3	55.4	51.2

These values are in kOhms!!!

### Multiple MAX chips

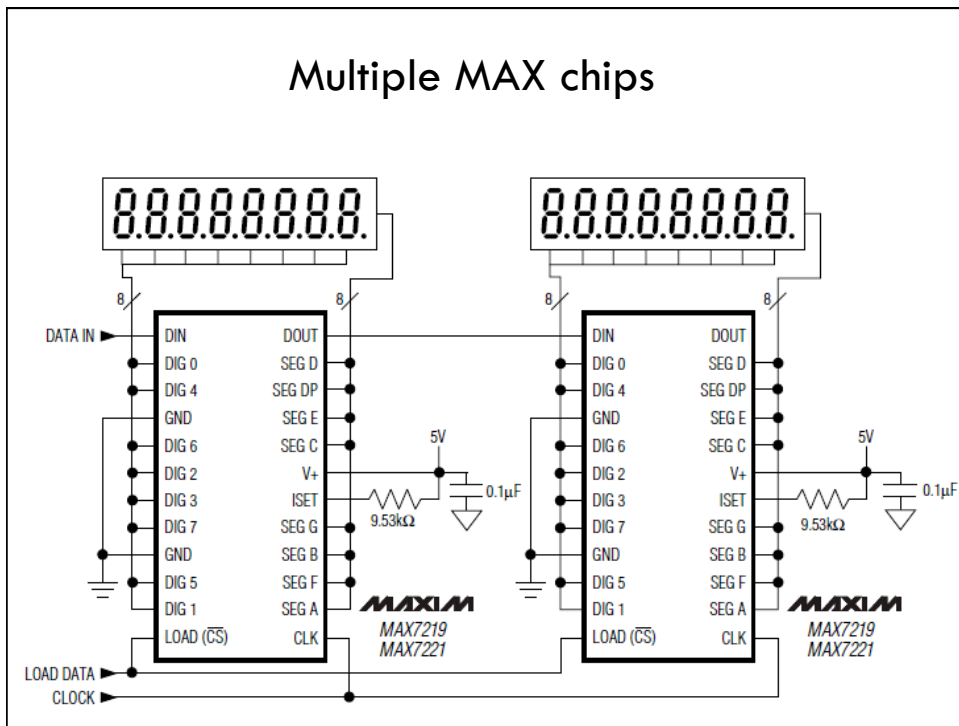

### Multiple MAX chips

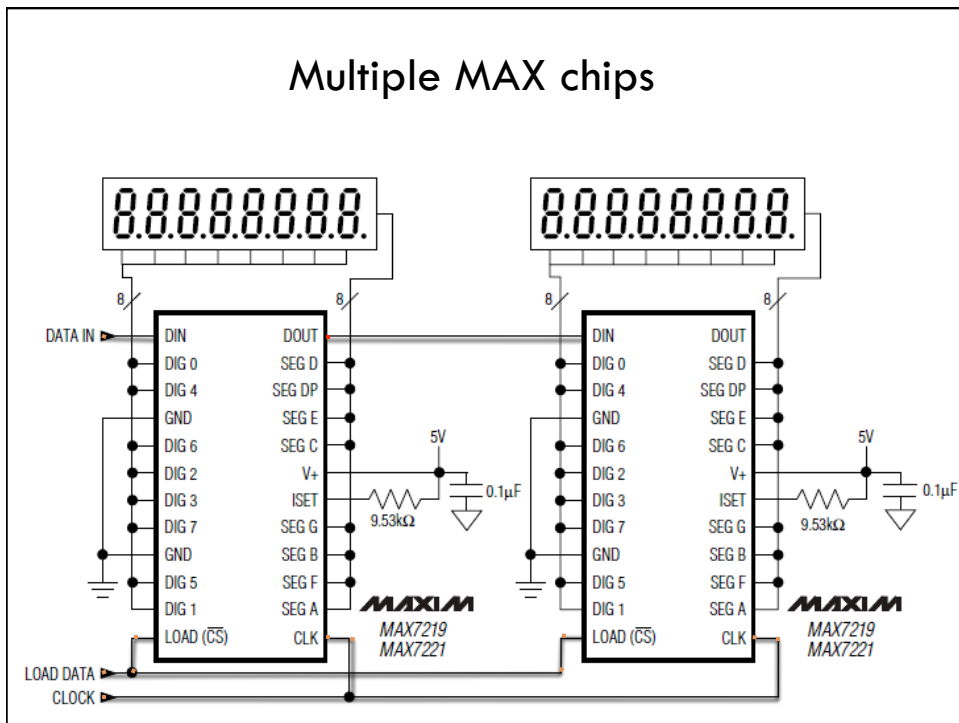


## Multiple MAX Chips

- There is an important difference between the way the `setRow()` and the `setColumn()` methods update the Leds:
  - `setRow()` only needs to send a single int-value to the MAX72XX in order to update all 8 Leds in a row.
  - `setColumn()` uses the `setLed()`-method internally to update the Leds. The library has to send 8 ints to the driver, so there is a performance penalty when using `setColumn()`.
  - You won't notice that visually when using only 1 or 2 cascaded Led-boards, but if you have a long queue of devices (6..8) which all have to be updated at the same time, that could lead to some delay that is actually visible.


## MAX 7219 Summary

- Drives lots more LEDs than the STP08DP05
  - 64 LEDs total
  - Designed for common-cathode LED arrays
    - Set the anodes to true and false
    - Pull down the cathodes in sequence
  - Uses time-multiplexing to drive them all
- Also supports 7-segment displays
  - Slightly more complex interface


## MAX7219 demo

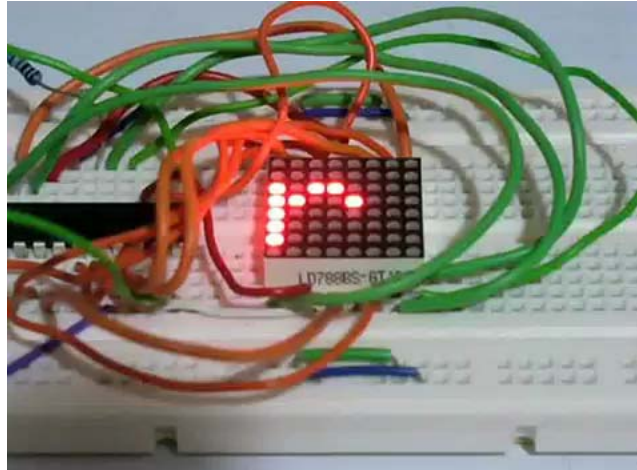


## MAX7219 demo

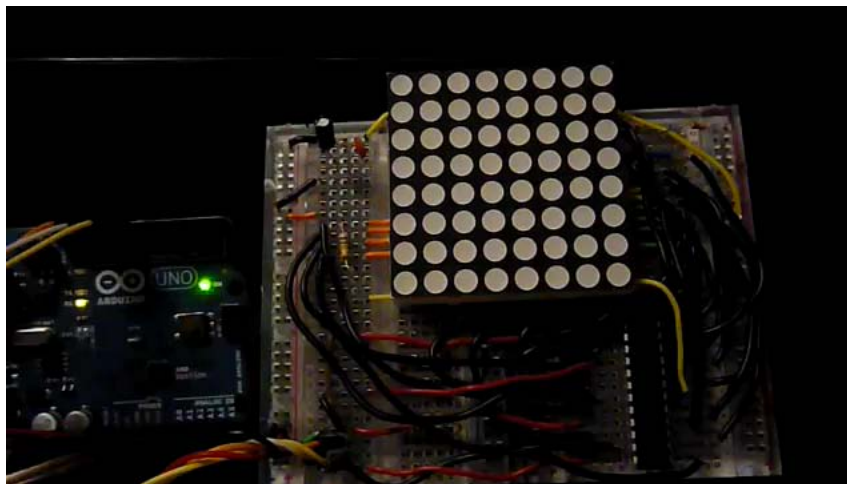

## MAX7219 demo

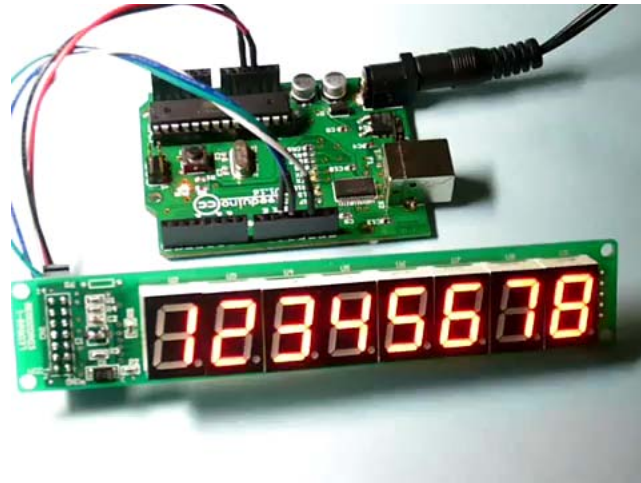

## MAX7219 demo

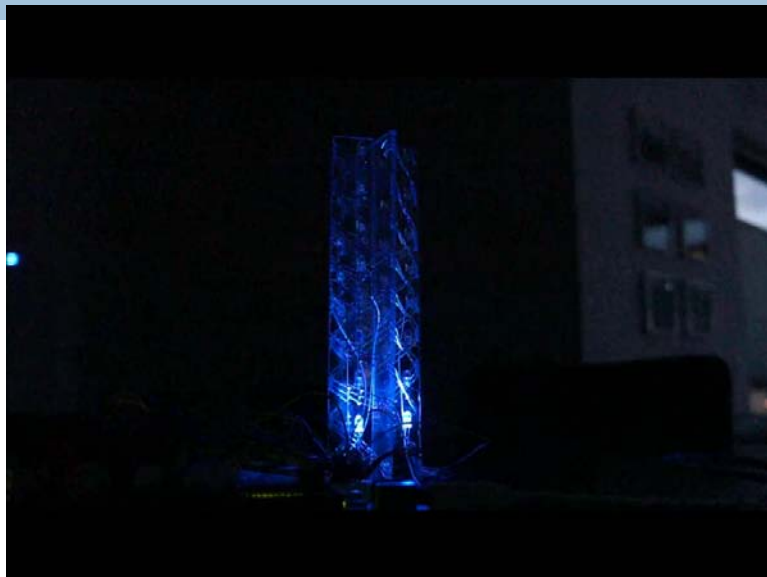

## Activity

- Write some Arduino code to make a pattern on an 8x8 LED array
  - You can wire one up if you like
    - We have LED matrices and Max7219 chips
    - Around 20 wires to add...
  - Or you can use one of mine
    - Pre-wired
    - Get practice writing code that drives the display

## Atmel SPI Support

- The Atmel ATmega328 chip supports hardware-controlled SPI
  - Could be faster than `shiftOut()` function
  - Uses built-in SPI register on ATmega328
    - Set up the SPI functionality by setting bits in a control register
    - Write data to the SPI output register (MOSI) which causes the transfer to happen
    - A bit gets set in the control register when it's done
    - Fixed pin assignments (`shiftOut()` can use any pins)



# Atmel SPI Support

Figure 18-1. SPI Block Diagram<sup>(1)</sup>


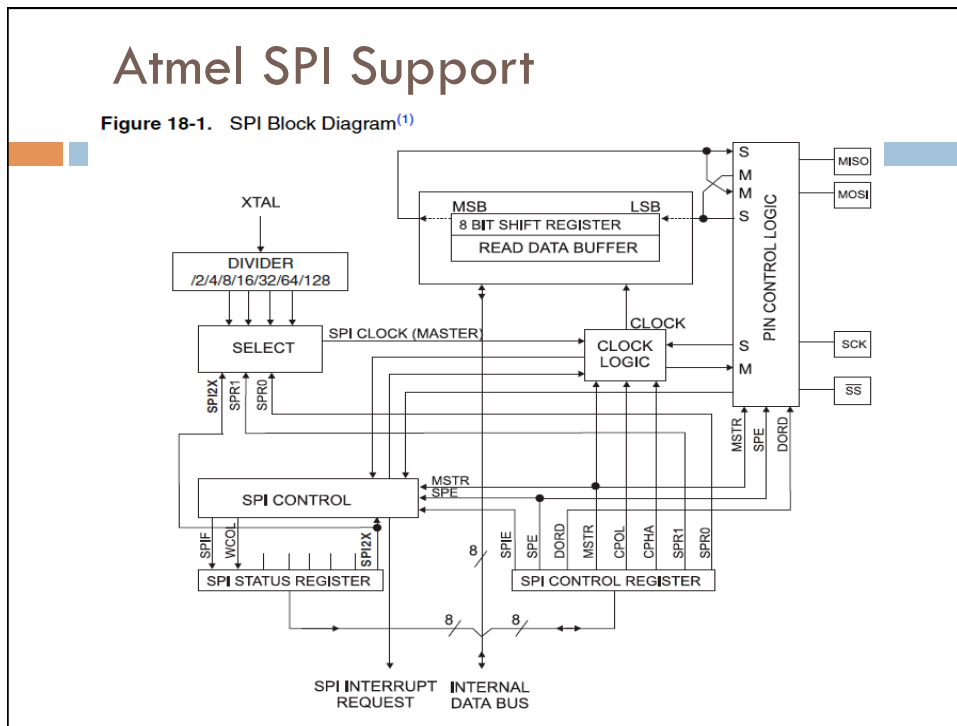


Figure 3: SPI - Single Master, Multiple Slaves

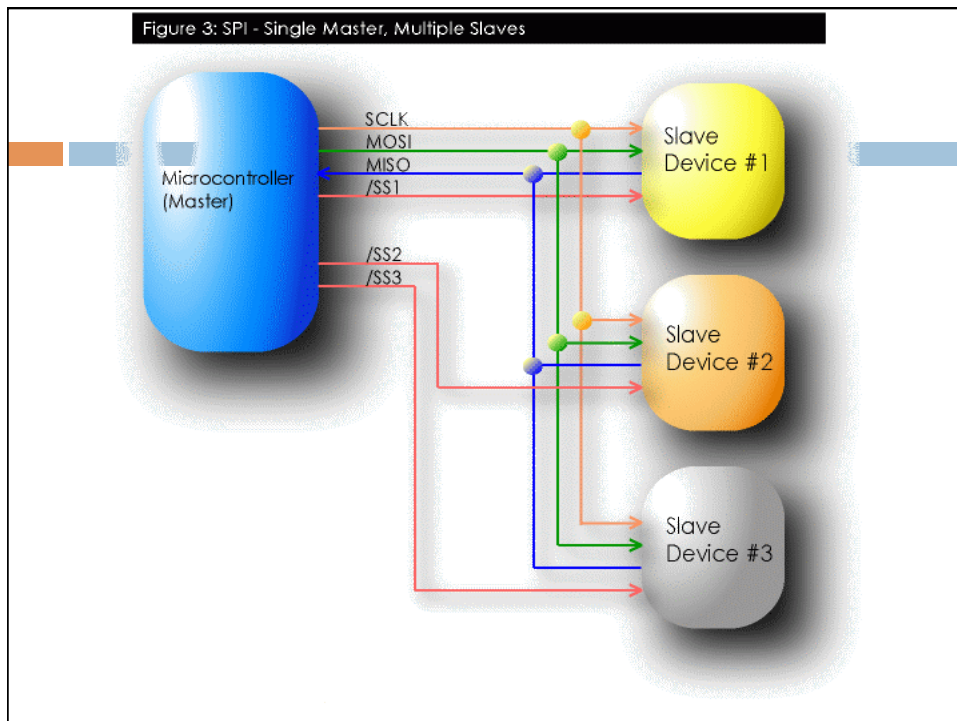

## SPI library setup

### Spi Library

This library provides functions for transferring information using the Serial Peripheral Interface (SPI). The SPI interface is automatically initialized when the Spi library is included in a sketch. It sets the following digital I/O pins:

```
pin 13 SCK    SPI clock
pin 12 MISO   SPI master in, slave out
pin 11 MOSI   SPI master out, slave in
pin 10 SS     SPI slave select
```

The default SPI configuration is as follows:

```
SPI Master enabled
MSB of the data byte transmitted first
SPI mode 0 (CPOL = 0, CPHA = 0)
SPI clock frequency = system clock / 4
```

## SPI Library Usage

```
#include <SPI.h>           // include library
int SS = 10;               // define Slave Select pin
In setup: pinMode(SS, OUTPUT); // SS must be output
                SPI.begin();    // init the library
                SPI.setBitOrder(MSBFIRST); // modify bit order

To use: SPI.transfer(byte); // transfer one byte
        n = SPI.transfer(byte) // returns bytes from slave
```

## Transfer a byte using SPI

```

char spi_transfer(volatile char data) {
    SPDR = data ;                // start transmission
    while (!(SPSR & (1<<SPIF))) // wait for transmission
        { } ;                   // to finish (SPIF bit flag)
    return SPDR;                // return received byte
}

```

Magic stuff happens here: By writing data to the SPDR register, the SPI transfer is started. When the transfer is complete, the system raises the SPIF bit in the SPSR status register. The data that comes back from the slave is in SPDR when you're finished.

## SPI Details

### 18.5.1 SPCR – SPI Control Register

Bit	7	6	5	4	3	2	1	0	
0x2C (0x4C)	SPIE	SPE	DORD	MSTR	CPOL	CPHA	SPR1	SPR0	SPCR
Read/Write	R/W	R/W	R/W	R/W	R/W	R/W	R/W	R/W	
Initial Value	0	0	0	0	0	0	0	0	

- **Bit 7 – SPIE: SPI Interrupt Enable**

This bit causes the SPI interrupt to be executed if SPIF bit in the SPSR Register is set and the if the Global Interrupt Enable bit in SREG is set.

- **Bit 6 – SPE: SPI Enable**

When the SPE bit is written to one, the SPI is enabled. This bit must be set to enable any SPI operations.

- **Bit 5 – DORD: Data Order**

When the DORD bit is written to one, the LSB of the data word is transmitted first.

When the DORD bit is written to zero, the MSB of the data word is transmitted first.

- **Bit 4 – MSTR: Master/Slave Select**

This bit selects Master SPI mode when written to one, and Slave SPI mode when written logic zero. If  $\overline{SS}$  is configured as an input and is driven low while MSTR is set, MSTR will be cleared, and SPIF in SPSR will become set. The user will then have to set MSTR to re-enable SPI Master mode.

## SPI Details

- **Bit 3 – CPOL: Clock Polarity**

When this bit is written to one, SCK is high when idle. When CPOL is written to zero, SCK is low when idle. Refer to [Figure 18-3](#) and [Figure 18-4](#) for an example. The CPOL functionality is summarized below:

**Table 18-3.** CPOL Functionality

CPOL	Leading Edge	Trailing Edge
0	Rising	Falling
1	Falling	Rising

- **Bit 2 – CPHA: Clock Phase**

The settings of the Clock Phase bit (CPHA) determine if data is sampled on the leading (first) or trailing (last) edge of SCK. Refer to [Figure 18-3](#) and [Figure 18-4](#) for an example. The CPHA functionality is summarized below:

**Table 18-4.** CPHA Functionality

CPHA	Leading Edge	Trailing Edge
0	Sample	Setup
1	Setup	Sample

## SPI Details

- **Bits 1, 0 – SPR1, SPR0: SPI Clock Rate Select 1 and 0**

These two bits control the SCK rate of the device configured as a Master. SPR1 and SPR0 have no effect on the Slave. The relationship between SCK and the Oscillator Clock frequency  $f_{osc}$  is shown in the following table:

**Table 18-5.** Relationship Between SCK and the Oscillator Frequency

SPI2X	SPR1	SPR0	SCK Frequency
0	0	0	$f_{osc}/4$
0	0	1	$f_{osc}/16$
0	1	0	$f_{osc}/64$
0	1	1	$f_{osc}/128$
1	0	0	$f_{osc}/2$
1	0	1	$f_{osc}/8$
1	1	0	$f_{osc}/32$
1	1	1	$f_{osc}/64$

## SPI Details

### SPSR – SPI Status Register

Bit	7	6	5	4	3	2	1	0	
0x2D (0x4D)	SPIF	WCOL	–	–	–	–	–	SPI2X	SPSR
Read/Write	R	R	R	R	R	R	R	R/W	
Initial Value	0	0	0	0	0	0	0	0	

- **Bit 7 – SPIF: SPI Interrupt Flag**

When a serial transfer is complete, the SPIF Flag is set. An interrupt is generated if SPIE in SPCR is set and global interrupts are enabled. If  $\overline{SS}$  is an input and is driven low when the SPI is in Master mode, this will also set the SPIF Flag. SPIF is cleared by hardware when executing the corresponding interrupt handling vector. Alternatively, the SPIF bit is cleared by first reading the SPI Status Register with SPIF set, then accessing the SPI Data Register (SPDR).

- **Bit 6 – WCOL: Write COLLision Flag**

The WCOL bit is set if the SPI Data Register (SPDR) is written during a data transfer. The WCOL bit (and the SPIF bit) are cleared by first reading the SPI Status Register with WCOL set, and then accessing the SPI Data Register.

- **Bit 0 – SPI2X: Double SPI Speed Bit**


When this bit is written logic one the SPI speed (SCK Frequency) will be doubled when the SPI is in Master mode (see [Table 18-5](#)). This means that the minimum SCK period will be two CPU clock periods. When the SPI is configured as Slave, the SPI is only guaranteed to work at  $f_{osc}/4$  or lower.

## SPI Summary


- Very general way to send serial information from Arduino to another chip
  - DIY version: ShiftOut
    - use any pins
  - Fancy version: SPI library
    - uses fixed pins
  - Both do pretty much the same thing
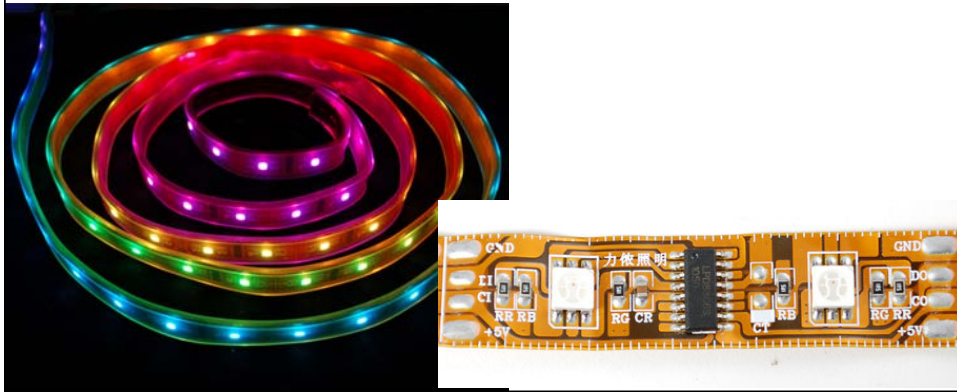
## Example LED “tape”


- RGB LEDs on a long tape
  - ▣ individually addressable and writable using SPI
  - ▣ 32 RGB LEDs per Meter (\$35/meter at Adafruit)



## Example LED “tape”

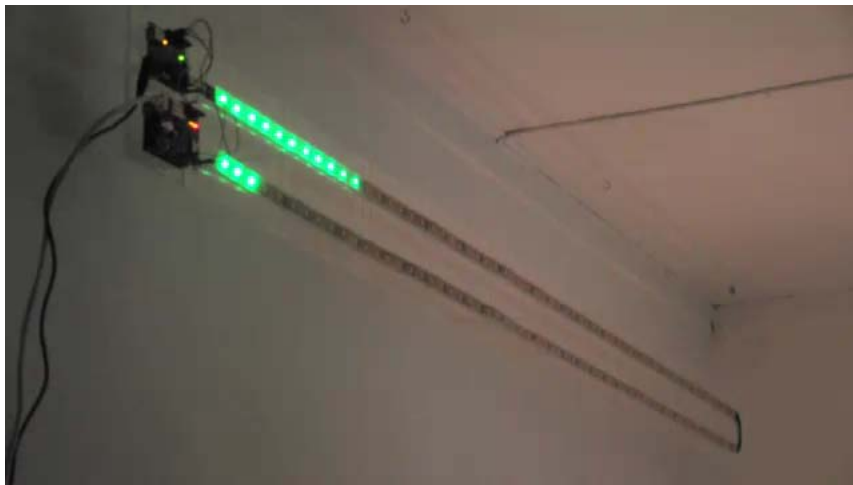

## Example LED "tape"

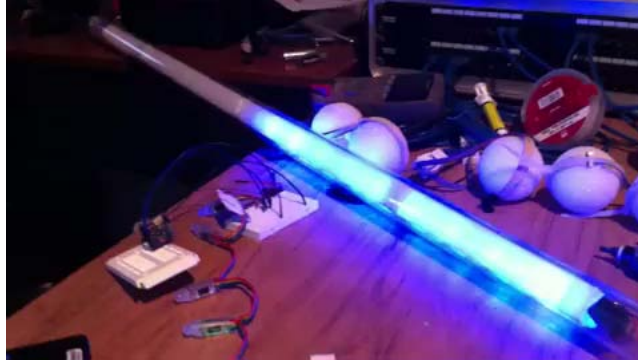

## Example LED "tape"



## SPI Summary

- Very general way to send serial information from Arduino to another chip
  - DIY version: ShiftOut
    - use any pins
  - Fancy version: SPI library
    - uses fixed pins
  - Both do pretty much the same thing
- Make sure your chip “speaks” SPI
  - If it “speaks” I<sup>2</sup>C, a whole different ball of wax...


## I<sup>2</sup>C – a.k.a. TWI

- Uses only two wires to communicate
  - Simpler?
- Each wire is bidirectional
- Can address up to 128 devices on a single I<sup>2</sup>C bus
  - Actually more complex...


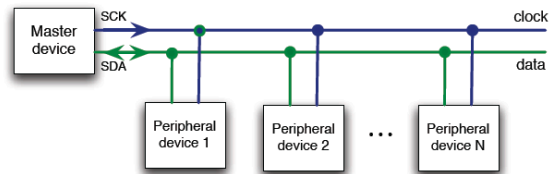
## I2C – a.k.a. TWI

Synchronous serial bus with shared a data line  
*a little network for your gadgets*



- Up to 127 devices on one bus
- Up to 1Mbps data rate
- Really simple protocol (compared to USB, Ethernet, etc)
- Most microcontrollers have it built-in


Tod Kurt: todbot.com

## I2C – a.k.a. TWI

### 21.2 2-wire Serial Interface Bus Definition

The 2-wire Serial Interface (TWI) is ideally suited for typical microcontroller applications. The TWI protocol allows the systems designer to interconnect up to 128 different devices using only two bi-directional bus lines, one for clock (SCL) and one for data (SDA). The only external hardware needed to implement the bus is a single pull-up resistor for each of the TWI bus lines. All devices connected to the bus have individual addresses, and mechanisms for resolving bus contention are inherent in the TWI protocol.

Figure 21-1. TWI Bus Interconnection

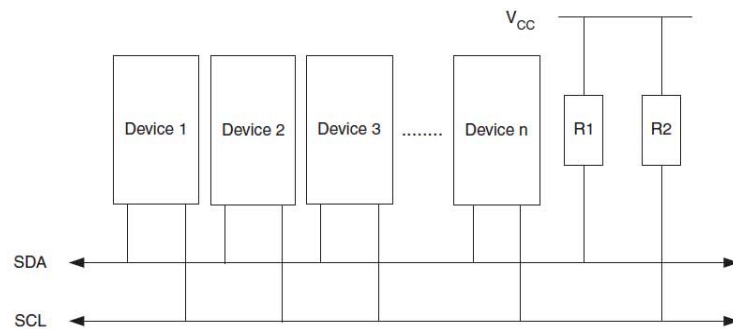


**21.2 2-wire Serial Interface Bus Definition**

The 2-wire Serial Interface (TWI) is ideally suited for typical microcontroller applications. The TWI protocol allows the systems designer to interconnect up to 128 different devices using only two bi-directional bus lines, one for clock (SCL) and one for data (SDA). The only external hardware needed to implement the bus is a single pull-up resistor for each of the TWI bus lines. All devices connected to the bus have individual addresses, and mechanisms for resolving bus contention are inherent in the TWI protocol.

**Figure 21-1. TWI Bus Interconnection**

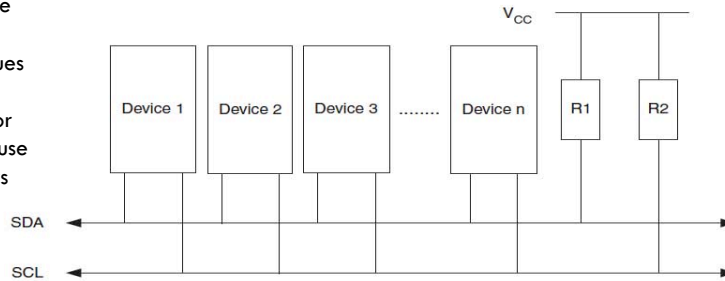1.8k, 4.7k, 10k are commonly used pullup resistor values


The wire library for Arduino can even use the built-in resistors on the AVR




C <sub>i</sub> <sup>(1)</sup>	Capacitance for each I/O Pin		-	10	pF
f <sub>SCL</sub>	SCL Clock Frequency	f <sub>CK</sub> <sup>(4)</sup> > max(16f <sub>SCL</sub> , 250kHz) <sup>(5)</sup>	0	400	kHz
R <sub>p</sub>	Value of Pull-up resistor	f <sub>SCL</sub> ≤ 100 kHz	$\frac{V_{CC}-0.4V}{3mA}$	$\frac{1000ns}{C_b}$	Ω
		f <sub>SCL</sub> > 100 kHz	$\frac{V_{CC}-0.4V}{3mA}$	$\frac{300ns}{C_b}$	Ω

**Address vs. Data**

**Figure 21-4. Address Packet Format**

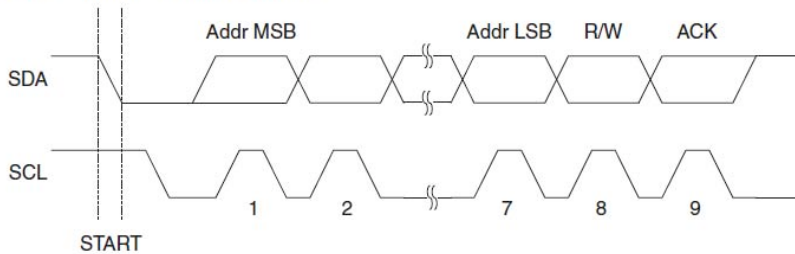


**Figure 21-5. Data Packet Format**

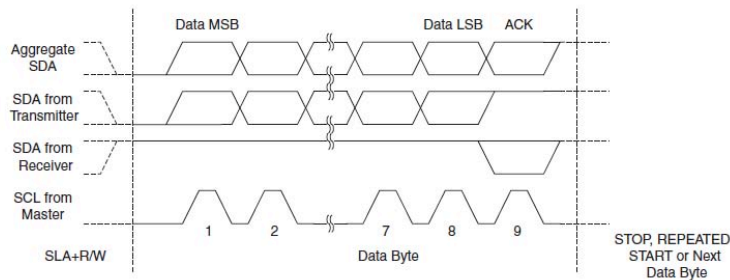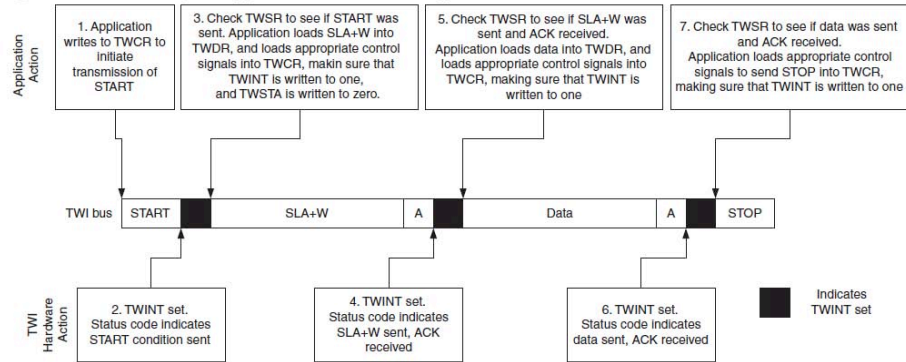

## Using I2C/TWI

Figure 21-10. Interfacing the Application to the TWI in a Typical Transmission



Luckily Arduino comes with an I2C library!

## Wire Library

[Buy](#) | [Download](#) | [Getting Started](#) | [Learning](#) | [Reference](#) | [Hardware](#) | [FAQ](#)

[Blog »](#) | [Forum »](#) | [Playground »](#)

[Reference](#) | [Language \(extended\)](#) | [Libraries](#) | [Comparison](#) | [Changes](#)

### Wire Library

This library allows you to communicate with I2C / TWI devices. On most Arduino boards, SDA (data line) is on analog input pin 4, and SCL (clock line) is on analog input pin 5. On the Arduino Mega, SDA is digital pin 20 and SCL is 21.

#### Functions

- `begin()`
- `begin(address)`
- `requestFrom(address, count)`
- `beginTransaction(address)`
- `endTransmission()`
- `send()`
- byte `available()`
- byte `receive()`
- `onReceive(handler)`
- `onRequest(handler)`

#### Note

There are both 7- and 8-bit versions of I2C addresses. 7 bits identify the device, and the eighth bit determines if it's being written to or read from. The Wire library uses 7-bit addresses throughout. If you have a datasheet or sample code that uses 8-bit addresses, you'll want to drop the low bit (i.e. shift the value one bit to the right), yielding an address between 0 and 127.

```

#include <Wire.h>
// TWI (I2C) sketch to communicate with the LIS3LV02DQ accelerometer
// Using the Wire library (created by Nicholas Zambetti)
// On the Arduino board, Analog In 4 is SDA, Analog In 5 is SCL
// The Wire class handles the TWI transactions, abstracting the nitty-gritty to make
// prototyping easy.
void setup(){
  pinMode(9, OUTPUT);
  digitalWrite(9, HIGH);
  Serial.begin(9600);

  Wire.begin(); // join i2c bus (address optional for master)
  Wire.beginTransmission(0x1D);
  Wire.send(0x20); // CTRL_REG1 (20h)
  Wire.send(0x87); // Device on, 40hz, normal mode, all axis's enabled
  Wire.endTransmission();
}
// Switch to Wii Nunchuck Slides!

```


## Wii Nunchuck Controller

- Standard I2C interface
- 3-axis accelerometer with 10-bit accuracy
- 2-axis analog joystick with 8-bit A/D converter
- 2 buttons
- \$20



Tod Kurt: todbot.com

## Wii Nunchuck Controller

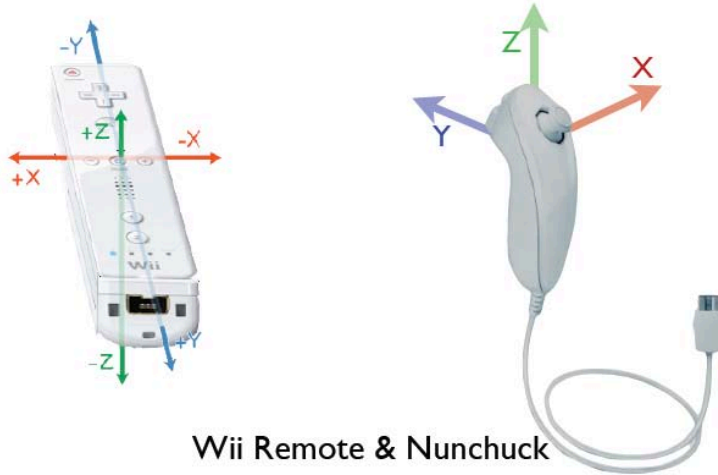


Wii Remote & Nunchuck  
accelerometer axes

Tod Kurt: todbot.com
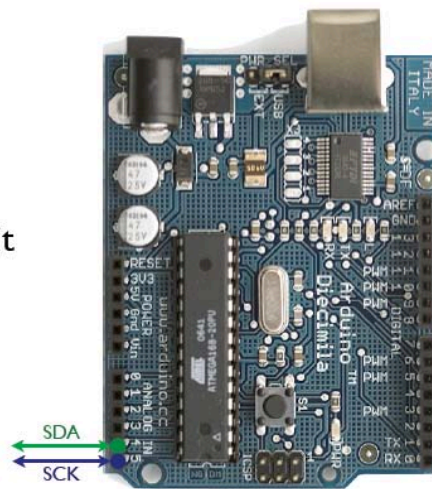
## I<sup>2</sup>C on Arduino


- I<sup>2</sup>C built-in on Arduino's ATmega328 chip
- Use "Wire" library to access it
- Analog In 4 is SDA signal
- Analog In 5 is SCK signal



Tod Kurt: todbot.com

## Arduino Wire Library


### Writing Data

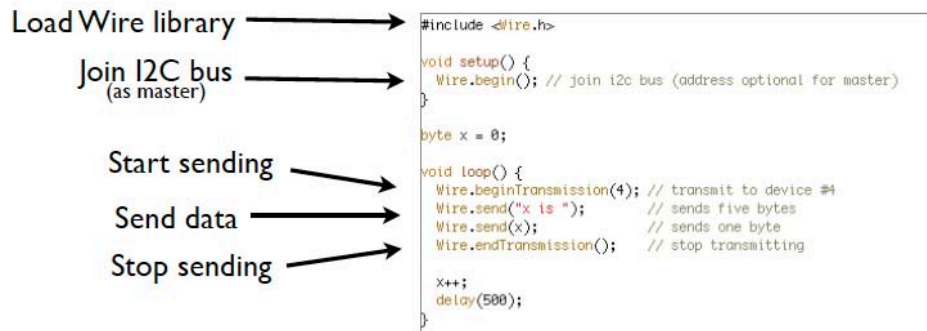

Tod Kurt: todbot.com

## Arduino Wire Library


### Reading Data

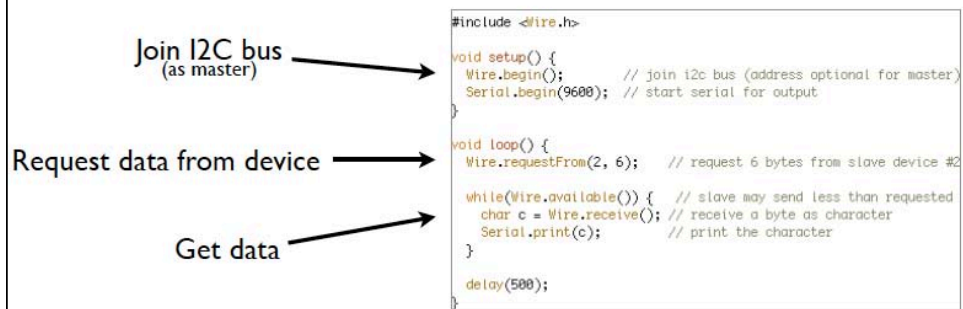

Tod Kurt: todbot.com
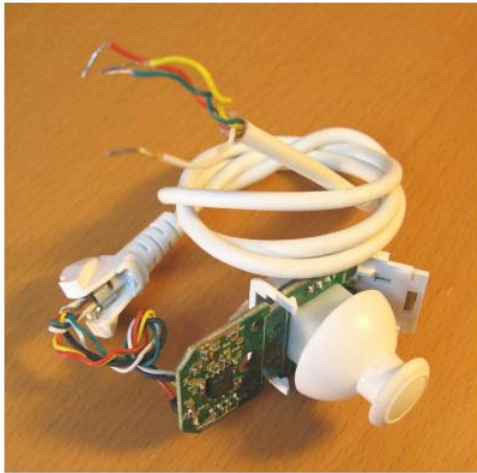
## Connecting to the Nunchuck

We could hack off the connector and use the wires directly




But instead let's use this little adapter board



Tod Kurt: todbot.com


## Connecting to the Nunchuck

Nunchuck Pinout

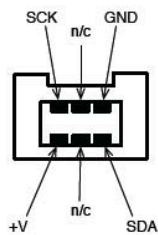

(looking into Nunchuck connector)


Adapter Pinout

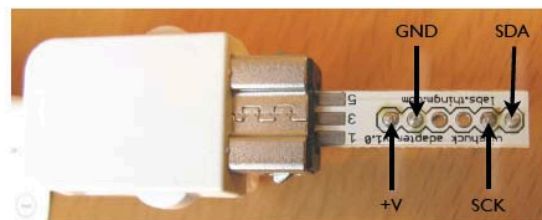

Tod Kurt: todbot.com



## Connecting to the Nunchuck

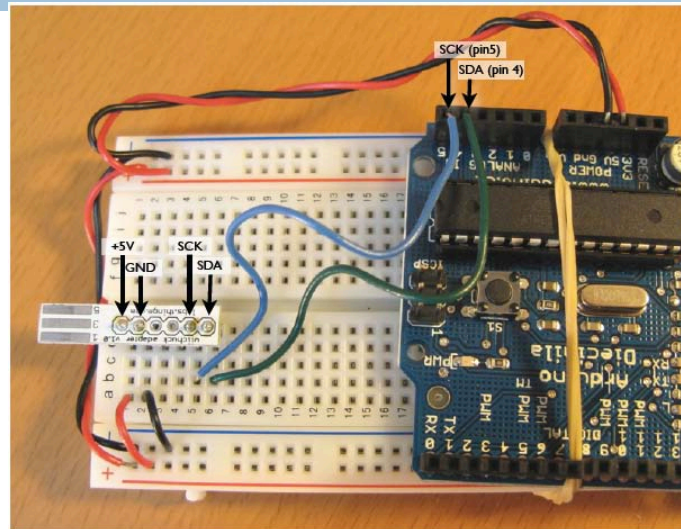


Tod Kurt: todbot.com

## Connecting to the Nunchuck
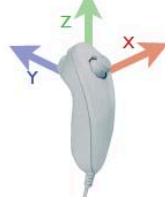
### “NunchuckPrint”

Read the Nunchuck every 1/10th of a second & print out all the data:

- joystick position (x,y)
- accelerometer (x,y,z)
- buttons Z,C



```

Arduino - 0010 Alpha
NunchuckPrint
#include <Wire.h>

void setup()
{
  Serial.begin(19200);
  nunchuck_init(); // send the initialization handshake
  Serial.print ("Finished setup\n");
}

void loop()
{
  nunchuck_get_data();
  nunchuck_print_data();
  delay(100);
}

```

19200 baud | Send

```

176   Joy:123,130   acc:141,160,178   but:1,1
177   Joy:123,130   acc:141,160,176   but:1,1
178   Joy:123,130
9

```

Tod Kurt: todbot.com



## Connecting to the Nunchuck

- Use Tod Kurt's library  
<http://todbot.com/blog/2008/02/18/wiichuck-wii-nunchuck-adapter-available/>
- or WiiChuck library from Arduino playground
- or info at  
<http://www.windmeadow.com/index.php?q=node/42>
- or library at  
<http://www.gabrielbianconi.com/projects/arduinonunchuk>

Tod Kurt: todbot.com

## Connecting to the Nunchuck

“NunchuckServo”

Move the servo by  
moving your arm

You're a cyborg!

Also press the Z button to  
flash the pin 13 LED

```

void checkNunchuck()
{
  if( loop_cnt > 100 ) { // loop()s is every 1msec, this is every 100ms
    nunchuck_get_data();
    nunchuck_print_data();

    float tilt = nunchuck_accelx(); // x-axis, in this case range
    tilt = (tilt - 70) * 1.5; // convert to angle in degrees,
    pulseWidth = (tilt * 9) + minPulse; // convert angle to microsec

    loop_cnt = 0; // reset for
  }
  loop_cnt++;
}

```


Done uploading.  
Binary sketch size: 6548 bytes (of a 14336 byte maximum)


Tod Kurt: todbot.com

## Back to LEDs: Roll your Own Interface

- TLC 5940 – 16-output LED driver with PWM on each output
  - ▣ 12-bits of PWM = 4096 levels of brightness
  - ▣ 16 bits with 12-bits of PWM each = 192 bits to send for each change of the LEDs
  - ▣ Communicates with a serial protocol, so you can chain them together
  - ▣ BUT, it's not SPI or I2C!
    - Rats...

## TLC 5940

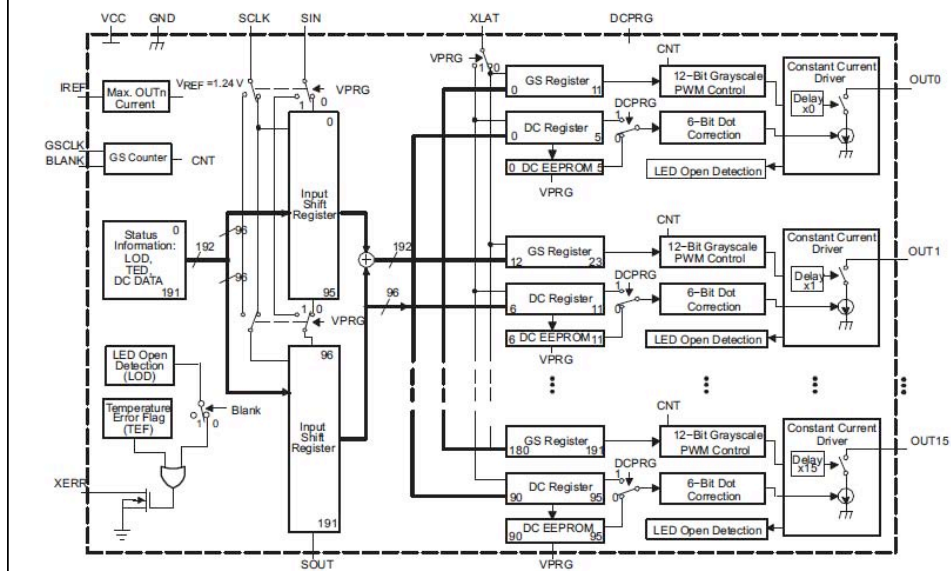

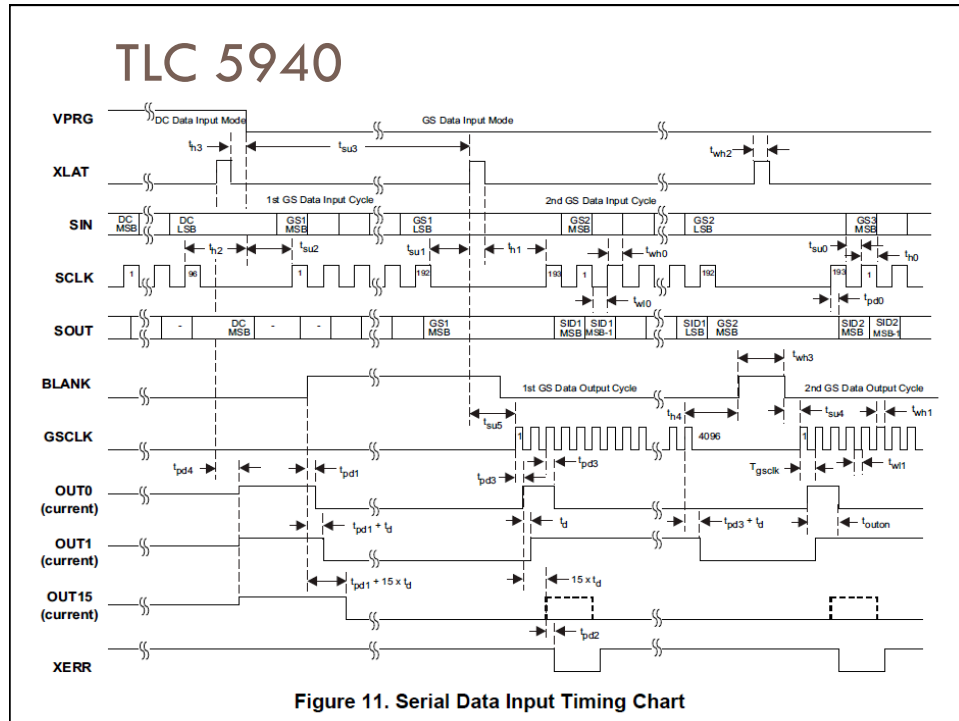

## PWM...

- Based on the “grayscale counter” which runs at a frequency that you send the chip

### GRAYSCALE PWM OPERATION

The grayscale PWM cycle starts with the falling edge of BLANK. The first GSCLK pulse after BLANK goes low increases the grayscale counter by one and switches on all  $OUT_n$  with grayscale value not zero. Each following rising edge of GSCLK increases the grayscale counter by one. The TLC5940 compares the grayscale value of each output  $OUT_n$  with the grayscale counter value. All  $OUT_n$  with grayscale values equal to the counter values are switched off. A BLANK=H signal after 4096 GSCLK pulses resets the grayscale counter to zero and completes the grayscale PWM cycle (see Figure 21). When the counter reaches a count of FFFh, the counter stops counting and all outputs turn off. Pulling BLANK high before the counter reaches FFFh immediately resets the counter to zero.


This means there are some relatively complex timings and relationships between the different signals that you have to get right

The Arduino 5940 library uses interrupt-driven control to get this right...

## PWM...
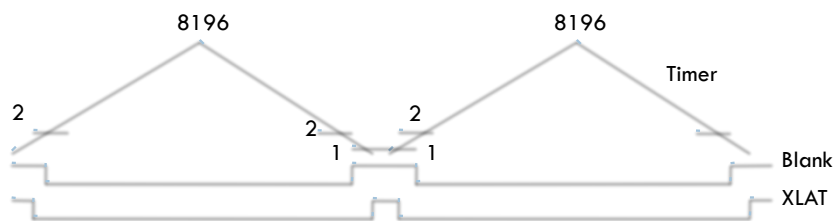
### GRAYSCALE PWM OPERATION

The grayscale PWM cycle starts with the falling edge of BLANK. The first GSCLK pulse after BLANK goes low increases the grayscale counter by one and switches on all OUTn with grayscale value not zero. Each following rising edge of GSCLK increases the grayscale counter by one. The TLC5940 compares the grayscale value of each output OUTn with the grayscale counter value. All OUTn with grayscale values equal to the counter values are switched off. A BLANK=H signal after 4096 GSCLK pulses resets the grayscale counter to zero and completes the grayscale PWM cycle (see [Figure 21](#)). When the counter reaches a count of FFFh, the counter stops counting and all outputs turn off. Pulling BLANK high before the counter reaches FFFh immediately resets the counter to zero.



## TLC5940 Library


First, for a serial interfaced part it has a rather large number of signals. Fortunately we can ignore many of them if we wish.

- XERR : open collector, wire or-ed output that lets you know a TLC5940 is over heated or has a burnt out LED. We can ignore this as it will always be on unless you have current using elements on all of the outputs.
- SOUT: serial data out from the TLC5940. Unless you wish to try to read the error bits you do not need this to come to the Arduino. If you have more than one TLC5940 this is the line you daisy chain to the SIN of the next package.
- DCPRG: this selects the source of the current limiter register, you could just tie it high.
- XLAT: you will need this to latch data after shifting.
- SCLK: you will need this to shift data.
- SIN: serial in to TLC5940, this is the output from the Arduino.
- VPRG: you need this to select either the current limit registers or the duty cycle registers for writing.
- GSCLK: this is the clock for the PWM. We will reprogram TIMER2 in the Arduino to make this signal. That will cost us the native PWM on that timer, digital 11 on a mega8, 11 and 3 on a mega168.
- BLANK: this marks the end of a PWM cycle in addition to blanking the output. We will reprogram TIMER1 to generate this signal. That will cost us the native PWMs on digital 9 and digital 10. (Tie a real, physical pull-up resistor on this line to keep things blanked while your Arduino boots. Depending on your hardware, it is possible that the TLC5940 would come up in a configuration that would dissipate too much power.)


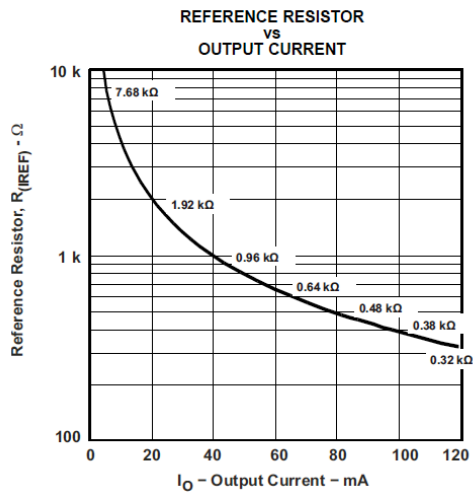
## TLC5940 – setting the resistor

- One resistor (to GND) sets current for all channels



Min = 5ma  
Max = 120ma

$$I_{\max} = \frac{V_{(IREF)}}{R_{(IREF)}} \times 31.5$$

where:


$$V_{(IREF)} = 1.24 \text{ V}$$

$$R_{(IREF)} = \text{User-selected external resistor.}$$
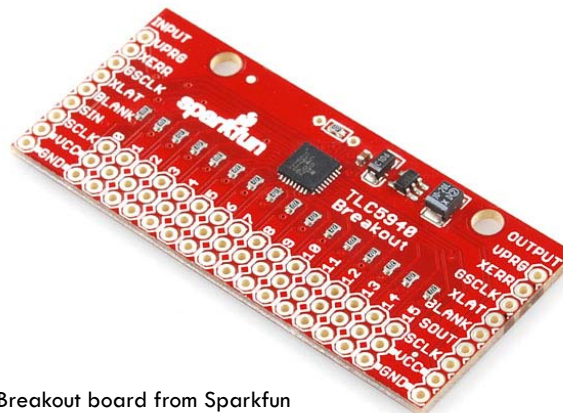
## TLC5940 Summary




- Easy to use – if you use the tlc5940 library!




Breakout board from Sparkfun  
\$13

## TLC5940 Examples

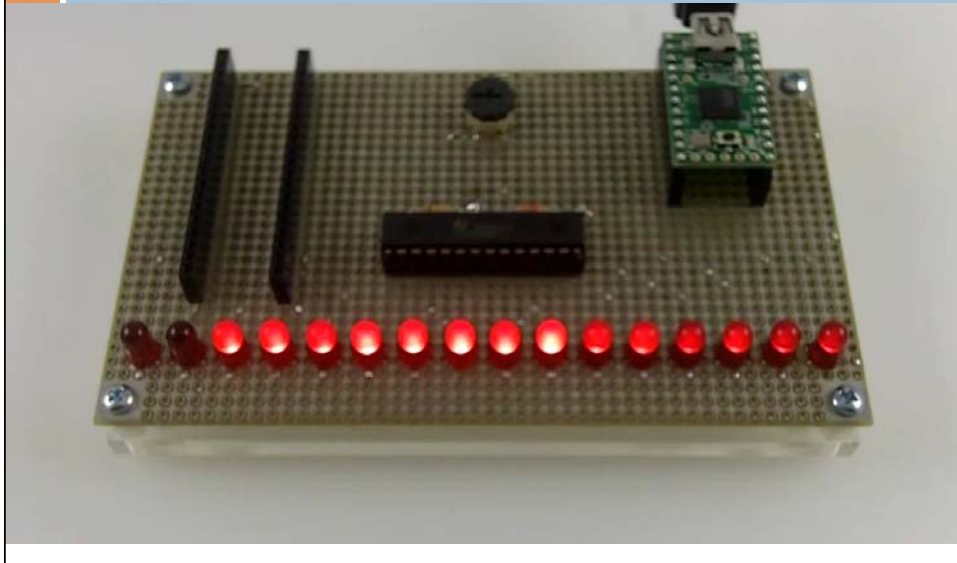

## TLC5940 Examples

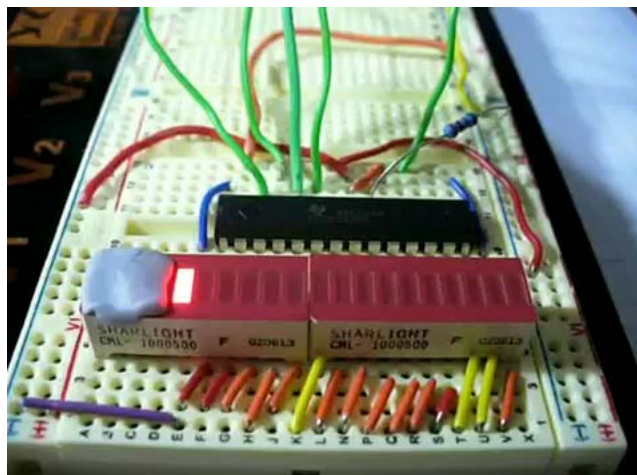



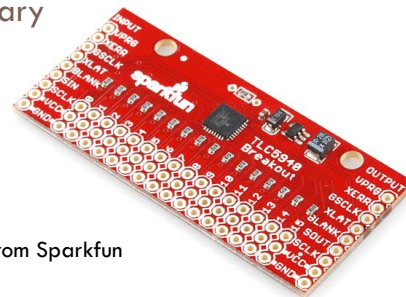
## TLC5940 Summary



- Easy to use – if you use the tlc5940 library!
- Can also use for servo control
  - ▣ Use the PWM channels to drive servos
  - ▣ Remember power issues!
  - ▣ Separate tlc5940 servo library
  - ▣ Resets some timing to get the servo timing right...



Breakout board from Sparkfun  
\$13

TLC servo functions. [More...](#)

```
#include <avr/io.h>
#include "Tlc5940.h"
```

[Go to the source code of this file.](#)

### Defines

#define	<b>SERVO_MAX_ANGLE</b>	180	The maximum angle of the servo.
#define	<b>SERVO_MIN_WIDTH</b>	204	The 1ms pulse width for zero degrees (0 - 4095).
#define	<b>SERVO_MAX_WIDTH</b>	410	The 2ms pulse width for 180 degrees (0 - 4095).
#define	<b>SERVO_TIMER1_TOP</b>	20000	The top value for XLAT and BLANK pulses.
#define	<b>SERVO_TIMER2_TOP</b>	77	The top value for GSCLK pulses.

### Functions

void	<b>tlc_initServos</b>	(uint8_t initAngle)	Initializes the tlc.
void	<b>tlc_setServo</b>	(TLC_CHANNEL_TYPE channel, uint8_t angle)	Sets a servo on channel to angle.
uint8_t	<b>tlc_getServo</b>	(TLC_CHANNEL_TYPE channel)	Gets the current angle that channel is set to.
uint16_t	<b>tlc_angleToVal</b>	(uint8_t angle)	Converts and angle (0 - SERVO_MAX_ANGLE) to the inverted tlc channel value (4095 - 0).
uint8_t	<b>tlc_valToAngle</b>	(uint16_t value)	Converts an inverted tlc channel value (4095 - 0) into an angle (0 - SERVO_MAX_ANGLE).



**Servos**

```

/*
  This sketch sweeps a servo on channel 0.

  To connect a servo:
  1. Put a 2k-5k pull-up resistor (R0 below; I've tried with 3.3k) between the
     servo control output pin and +5v.
  2. Connect that same pin to the servo's control line like so

  servo data pin
  |
  OUTn -----[-----]-----+5v
                R0

  Steve Pomeroy <steve ~AT~ staticfree.info>, 2009-01-20 */

#include "Tlc5940.h"
#include "tlc_servos.h"

#define SERVO_CHANNEL 0
#define DELAY_TIME 20

void setup()
{
  tlc_initServos(); // Note: this will drop the PWM frequency down to 50Hz.
}


void loop()
{
  for (int angle = 0; angle < 180; angle++) {
    tlc_setServo(SERVO_CHANNEL, angle);
    Tlc.update();
    delay(DELAY_TIME);
  }
  for (int angle = 180; angle >= 0; angle--) {
    tlc_setServo(SERVO_CHANNEL, angle);
    Tlc.update();
    delay(DELAY_TIME);
  }
}

```

## TLC5940 Servo Example




## Multiple Servo Breakout Board

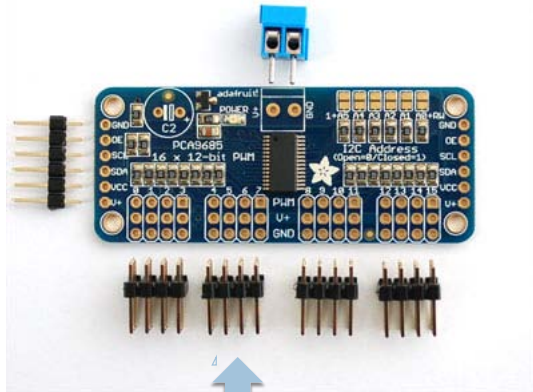

Control 16 servos with I<sup>2</sup>C to Arduino  
Can be chained for even more  
\$15 from Adafruit

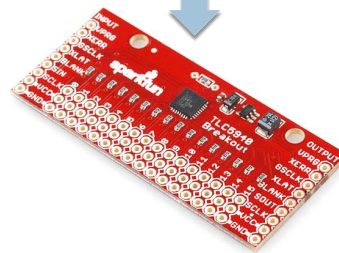TLC5940  
Breakout board from Sparkfun  
\$13



## External Chip Communication Summary

- There are lots of ways to interface with other chips
  - ▣ `shiftOut()` – simple serial
    - Output only
  - ▣ SPI – standard serial protocol – three wires CLK, DATA, En
    - Can be bi-directional
  - ▣ I<sup>2</sup>C / TWI – two wire protocol – requires a little more complex addressing and protocol, and pullup resistors
    - Can also be bidirectional
  - ▣ Non-standard serial – read the data sheet carefully!

## LED Driver Chips Summary

- **STP08DP05**
  - Drives 8 LEDs with constant-current sources (\$1.82)
  - SPI interface
- **MAX 7219/7221**
  - drives 8 digits of 7-segment display or 64 LEDs (8x8 array) (\$9.95)
  - Common-cathode LED arrays or digits – SPI interface
- **TLC5940/5941**
  - Drives 16 LEDs with each LED having 12 bits of PWM brightness (\$5.95)
  - Complicated communication protocol
  - Can also be used for multiple servos